



# AMITY UNIVERSITY

— UTTAR PRADESH —

## MODEL ANSWER

(End Semester Examination: April 2024)

Institution: Amity School of Engineering and Technology, Noida


Domain Name: Engineering & Technology

Stream Name: Electrical Engineering / Instrumentation Engineering


Course Code: ES103

Course Title: Basic Electrical Engineering

Model Answer Prepared By :

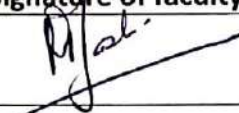
S. No.	Name of Faculty	Emp. Code	Signature of faculty
1	Mentab farim	0788	
2			

I confirm that the meeting of the above faculties has been convened.

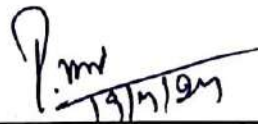  
19/4/24

Signature of HoI/HOD with Seal

— X — X — X — X

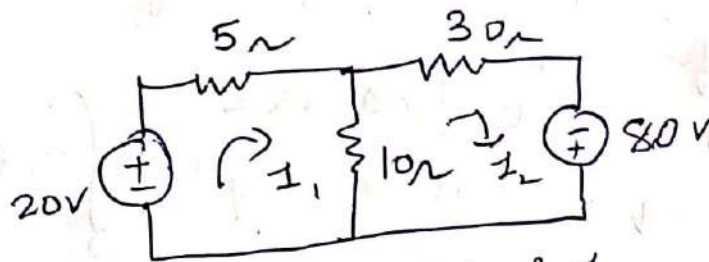Section ASoln 1 :

Assuming mesh currents  $I_1$  &  $I_2$   
KVL in mesh 1 is

$$20 - 5I_1 - 10(I_1 - I_2) = 0$$

$$20 - 15I_1 + 10I_2 = 0$$

$$15I_1 - 10I_2 = 20 \quad \text{--- (1)}$$

(2 marks)

KVL in mesh 2 is

$$-30I_2 + 80 - 10(I_2 - I_1) = 0$$

$$10I_1 - 40I_2 + 80 = 0$$

$$10I_1 - 40I_2 = -80 \quad \text{--- (2)}$$

(2 marks)


Solving (1) & (2)  $I_1 = 3.2$   $I_2 = 2.8$

Thus current through  $10\Omega = I_1 - I_2 = 3.2 - 2.8 = 0.4A$  (downward direction)

(2 marks)

Soln 2: Form factor: It is defined as ratio of  
RMS Value to average value.

(4 marks)

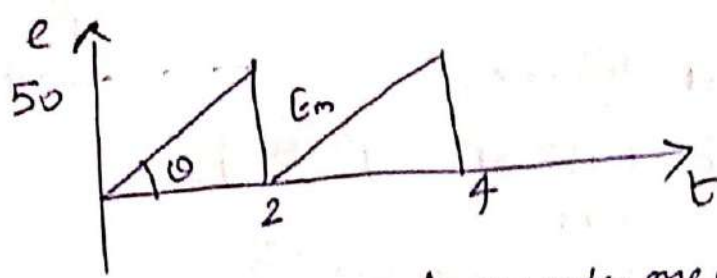

$$\text{Average value} = \frac{\text{Area under one cycle}}{\text{one cycle length}}$$

$$= \frac{\frac{1}{2} \times 2 \times 50}{2} = 25 \text{ volts.}$$

2 marks

$$\text{RMS value} = \sqrt{\frac{\text{Area of sq. wave under one cycle}}{\text{one cycle length}}}$$

Wave is defined as

$$e_1 = 25t \text{ for } 0 < t < 2$$

$$\therefore \text{Area of sq. wave under one cycle} = \int_0^2 e_1^2(t) dt$$

$$= \int_0^2 25^2 t^2 dt = 625 \left[ \frac{t^3}{3} \right]_0^2$$

$$= 625 \times \frac{8}{3} = 1666.67$$

$$\therefore \text{RMS value} = \sqrt{\frac{1666.67}{2}} = 28.87 \text{ volts.}$$

$$\therefore \text{Form factor} = \frac{\text{RMS value}}{\text{Avg value}} = \frac{28.87}{25} = 1.155$$

Soln 3: Shunts — low resistance in parallel with PMMC coil to increase the range of PMMC ammeter (2 marks)

Multiples — high resistance in series with PMMC coil to increase the range of PMMC voltmeter. (2 marks)

As given  $R_m = 5 \Omega$   
 $I_m = 15 \text{ mA}$

$$S = ? \quad I = 1 \text{ A}$$


$$S = \frac{I_m R_m}{I - I_m} = \frac{0.015 \times 5}{1 - 0.015} = 0.0761 \Omega$$

2 marks



Soln 4:

Page 3

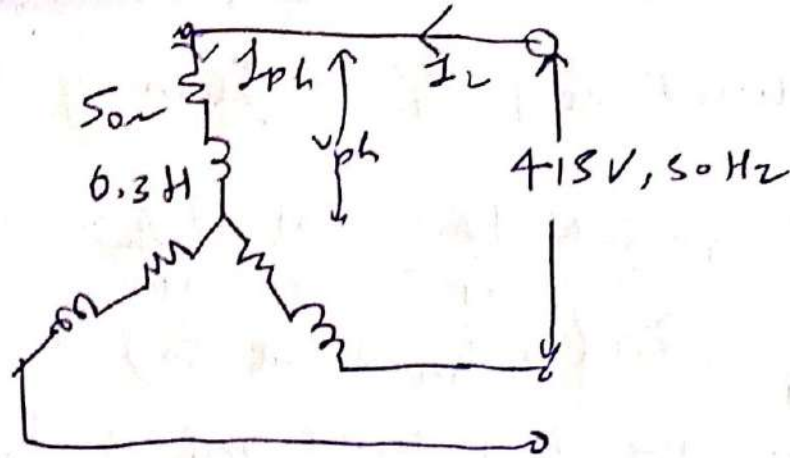

$$V_L = 415 \text{ V} \quad R_{ph} = 50 \Omega \quad L_{ph} = 0.3 \text{ H}$$

$$\therefore X_{ph} = \omega L_{ph} = 2\pi f \times L_{ph} = 2 \times 3.14 \times 50 \times 0.3 = 94.2 \Omega$$

$$\therefore Z_{ph} = \sqrt{R_{ph}^2 + X_{ph}^2} = \sqrt{50^2 + 94.2^2} = 106.65 \Omega$$

$$\Rightarrow I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{V_L / \sqrt{3}}{106.65} = \frac{415 / \sqrt{3}}{106.65} = 2.25 \text{ A}$$

$$\therefore I_L = I_{ph} = 2.25 \text{ A} \quad \text{--- (2 marks)}$$

$$\text{Power Consumed} = \sqrt{3} V_L I_L \cos \phi$$

$$\text{where } \cos \phi = \frac{R_{ph}}{Z_{ph}} = \frac{50}{106.65} = 0.468 \quad \text{(2 marks)}$$

$$\therefore P = \sqrt{3} V_L I_L \cos \phi = 756.89 \text{ Watts} \quad \text{(2 marks)}$$

Soln 5: EMF Eqn of transformer is given by

$$E_1 = 4.44 f \phi_m N_1$$

$$\& E_2 = 4.44 f \phi_m N_2$$

Derivation: Consider an AC supply of  $V_1$  & freq  $f$  is applied to primary side of transformer. The flux produced in primary is  $\phi_1 = \phi_m \sin \omega t$

Page 4

The induced emf  $e_1$  as primary as per Faraday's law is

$$e_1 = -N_1 \frac{d\phi}{dt} = -\frac{N_1}{\omega} \frac{d(\phi_m \sin \omega t)}{dt}$$

$$e_1 = 2\pi f N_1 \phi_m \sin(\omega t - 90^\circ) \quad \text{--- (1)}$$

The max value of induced emf is  $E_{m1} = 2\pi f N_1 \phi_m$   
RMS value is thus

$$E_1 = \frac{E_{m1}}{\sqrt{2}} = \frac{2\pi f N_1 \phi_m}{\sqrt{2}} = 4.44 f \phi_m N_1$$

Similarly  $E_2 = 4.44 f \phi_m N_2$  (4 marks)

Turns ratio is ratio of no of turns of secondary winding to no of turns of primary winding. (2 marks)

$$k = \frac{N_2}{N_1} = \frac{E_1}{E_2} = \text{turns ratio}$$

### Section B

Soln 6(a)  $X = 208 \Omega$   
 $R = 145 \Omega$

$V = 130 \text{ volts}$   
 $f = 60 \text{ Hz}$

$$X = \sqrt{R^2 + X_c^2}$$

$$X_c = \sqrt{X^2 - R^2}$$

$$= \sqrt{208^2 - 145^2} = 149.13 \Omega \quad \text{as } X_c = \frac{1}{2\pi f C}$$

(1)  $\therefore C = \frac{1}{X_c \times 2 \times 3.14 \times 60} = \frac{1}{149.13 \times 376.8} = 17.89 \text{ nF}$  (2 marks)

$P = VI \cos \phi \Rightarrow \text{where } \cos \phi = \frac{R}{X} = 0.697$  (4 marks)

$$I = \frac{V}{Z} = \frac{130}{208} = 0.625 \text{ A}$$

Page 5

(ii)  $\therefore P = 130 \times 0.625 \times 0.697$   
 $= \underline{56.63 \text{ W}}$

(2 marks)

6(b) Resonance is a condition in RLC <sup>series</sup> circuit when its power factor becomes unity i.e. voltage & current in the circuit are in phase. (2 marks)

Resonant frequency  $f_r = \frac{1}{2\pi\sqrt{LC}}$  (3 marks)

At resonance  $X_L = X_C$

$$\omega L = \frac{1}{\omega C}$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$


$$\Rightarrow \boxed{f_r = \frac{1}{2\pi\sqrt{LC}}}$$

Soln  
7(a) Power Measurement methods — three wattmeter method & its connection diagram (2 marks)  
 Two wattmeter method & its connection diagram (2 marks)

Two wattmeter method is preferred as method is independent of source unbalance, load unbalance, type of supply etc. (1 mark)



7(b)

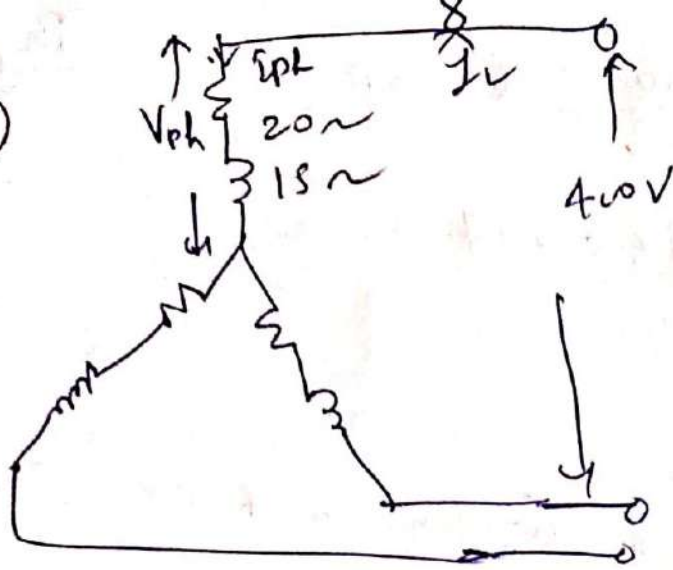

$$X_L = \omega L \Rightarrow f = \frac{X_L}{2\pi f} = \frac{15}{2 \times 3.14 \times 50} = 0.0474 \text{ H (1 mark)}$$


$$Z = \sqrt{R^2 + X_L^2} = \sqrt{20^2 + 15^2} = 25 \Omega \text{ (1 mark)}$$

$$I_L = I_{ph} = \frac{V_{ph}}{Z} = \frac{V_L / \sqrt{3}}{Z} = \frac{400 / \sqrt{3}}{25} = 9.23 \text{ A (1 mark)}$$

$$\cos \phi = \frac{R}{Z} = \frac{20}{25} = 0.8 \text{ (1 mark)}$$

$$P = \sqrt{3} V_L I_L \cos \phi = 5115.78 \text{ Watts}$$

Soln 8(a) DC Machines

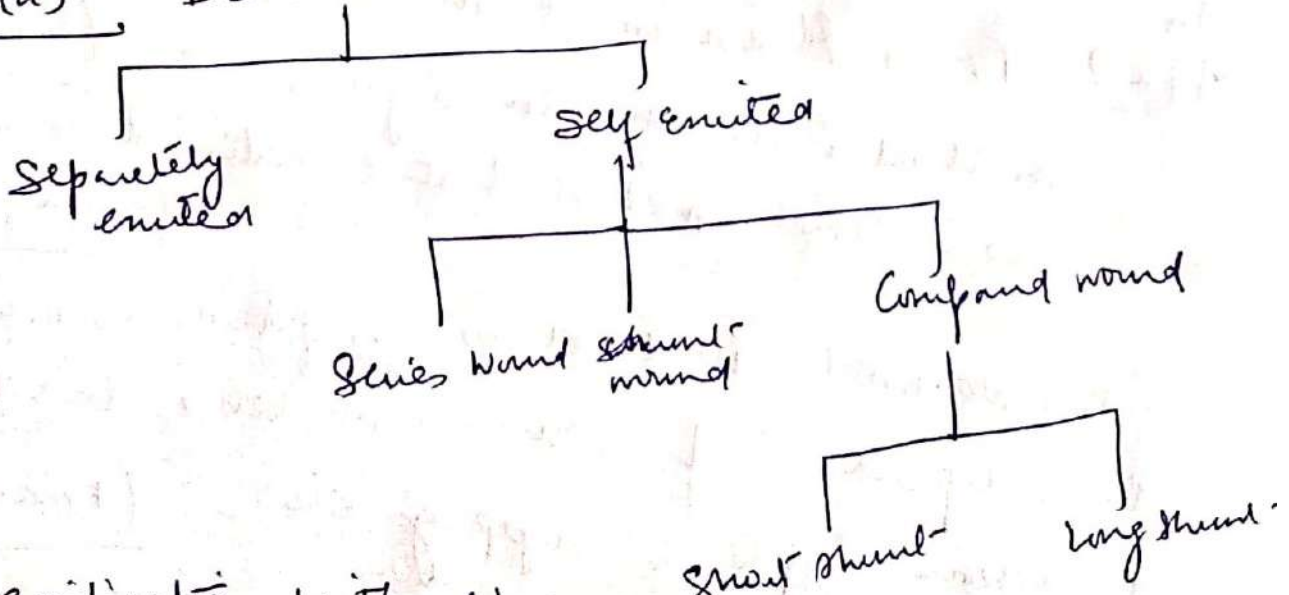


Classification with diagrams of each (3 marks)


# Different types of DC Motors

Page 7  
(3 marks)


## ① series Motor

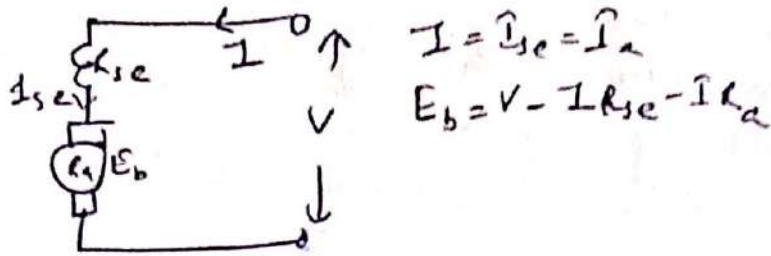


## ② Shunt Motor

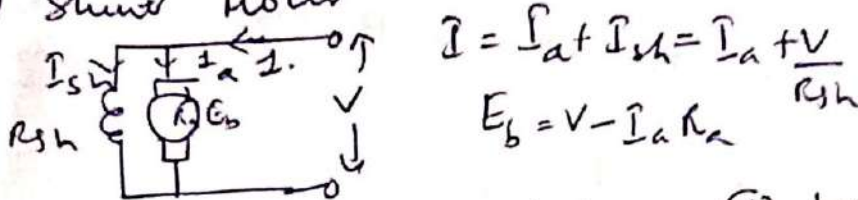

## ③ short shunt compound Motor

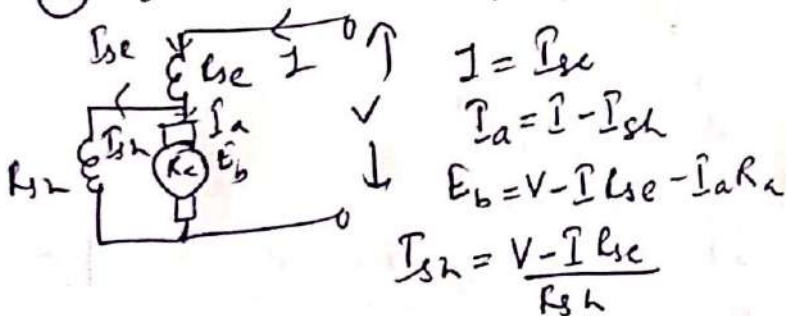

## ④ long shunt compound Motor

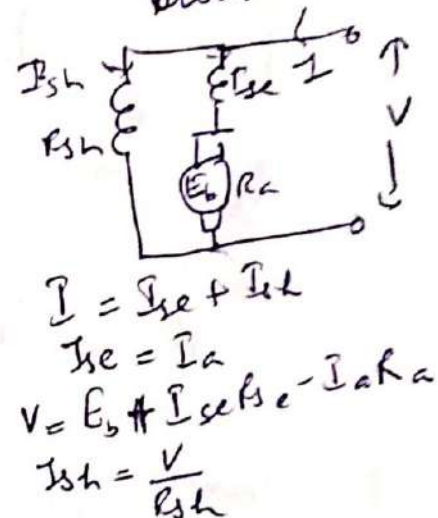


8(b)

$$I_L = 450 \text{ A}$$

$$V = 230 \text{ V}$$

$$R_{sh} = 50 \Omega$$

$$R_a = 0.03 \Omega$$

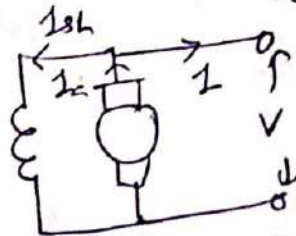

$$\text{As } E_g = V + I_a R_a$$

$$\text{and } I_a = I + I_{sh} = 450 + \frac{V}{R_{sh}} = 450 + \frac{230}{50} = 454.6 \text{ A}$$

$$\therefore E_g = V + I_a R_a$$

$$= 230 + 454.6 \times 0.03$$


$$E_g = 243.64 \text{ volts}$$

(4 marks)




Soln 9(a) PMMC Instrument  
 Construction with diagram — (2 marks)  
 Working explanation — (2 marks)  
 Merits & demerits — (2 marks)

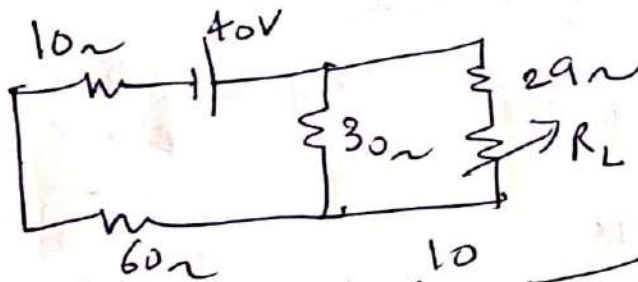9(b) Maximum Power Transfer Theorem — Statement (2 marks)



$R_L = R_{Th}$

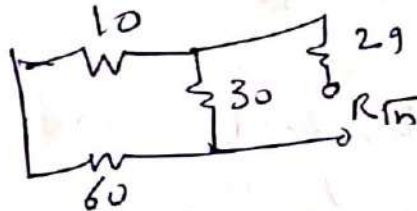


$$R_L = (10 \parallel 30) + 29 = 50\Omega$$

(4 marks)

(1 mark)

$$P_{max} = \frac{V_{Th}^2}{4R_L}$$

$V_{Th}$  calculation:

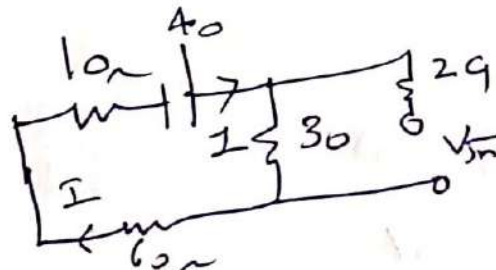


$$V_{Th} = \text{voltage across } 30\Omega = I \times 30 = \frac{40}{10+30+60} \times 30 = 12 \text{ volts}$$


$$\therefore P_{max} = \frac{V_{Th}^2}{4R_L} = \frac{12^2}{4 \times 50} = 0.72 \text{ Watts}$$

(4 marks)

9(c)

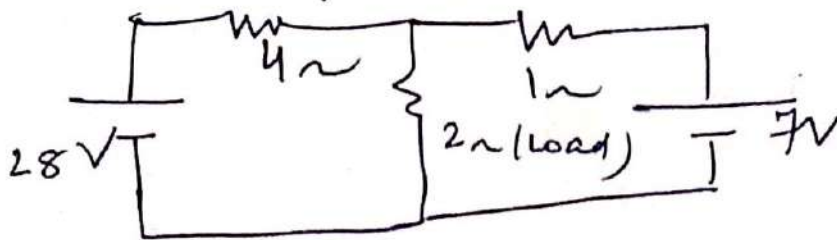


Norton's equivalent circuit is

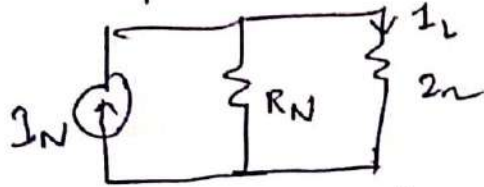


$$I_L = \frac{R_N}{R_N + 2} \times I_N \quad \text{--- (1)}$$

$R_N$  is

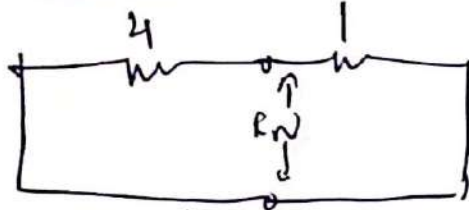

$$R_N = 4 \parallel 1 = \frac{4}{5} \Omega \quad \text{(1 mark)}$$

$I_N$  is

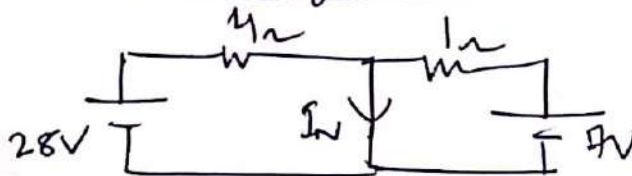

$$I_N = \frac{28}{4} + \frac{7}{1} = 14 \text{ A} \quad \text{(1 mark)}$$

Using eqn (1)

$$I_L = \frac{\frac{4}{5}}{\frac{4}{5} + 2} \times 14 = 4 \text{ A} \quad \text{(2 marks)}$$

\_\_\_\_\_ x \_\_\_\_\_ x End \_\_\_\_\_ x \_\_\_\_\_

*[Signature]*  
19/7/21

*[Signature]*  
Ms. Mehtab Fatima  
Employee id: 0488