

**MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY, WEST BENGAL**

Paper Code : ESC 301/ESC301/PC-ROB301 Analog and Digital Electronics

UPID : 003442

Time Allotted : 3 Hours

Full Marks : 70

*The Figures in the margin indicate full marks.**Candidate are required to give their answers in their own words as far as practicable***Group-A (Very Short Answer Type Question)**

1. Answer any ten of the following :

[1 × 10 = 10]

- (i) The functional difference between an S-R flip-flop and a J-K flip-flop is that
 - a) J-K flip-flop is faster than S-R flip-flop
 - b) J-K flip-flop has a feedback path
 - c) J-K flip-flop accepts both inputs equals to 1
 - d) J-K flip-flop does not require external clock
- (ii) Which of the following represents range of frequency measured by ADC?
 - a) Bandwidth
 - b) Threshold frequency
 - c) Peak frequency
 - d) None of the mentioned
- (iii) What is the maximum efficiency of a class B power amplifier?
 - a) 50% b) 90% c) 25% d) 78.5%
- (iv) How many Half adders required to add two 8 bit numbers?
 - (a) 8 (b) 15 (c) 10 (d) 2
- (v) The invalid state for S-R latch occurs when S and R are _____.
 - a) both high
 - b) both low
 - c) S = high, R = low
 - d) S = low, R = high
- (vi) Which A/D converter is considered to be simplest, fastest and most expensive? a) Servo converter b) Counter type ADC c) Flash type ADC d) none of the above.
- (vii) Where does the Q point lie for class B amplifier?
 - a) Active
 - b) Cut off
 - c) Saturation
 - d) Between saturation and active
- (viii) Which of the following combinations cannot be combined into K-map groups?
 - a) Overlapping combinations b) Diagonal corners c) Corners in the same column d) Corners in the same row
- (ix) A D flip-flop can be used as
 - a) divider circuit b) differentiator c) delay switch d) toggle circuit
- (x) The fastest logic gate family is
 - a) CMOS
 - b) ECL
 - c) TTL
 - d) RTL.
- (xi) For a Class B amplifier, the utilized load power is 300W and the DC power is 500W, find efficiency.
 - a) 30%
 - b) 60%
 - c) 90%
 - d) 100%
- (xii) An example of weighted code is
 - a) 2421 b) GRAY c) XS3 d) All of these

Group-B (Short Answer Type Question)

Answer any three of the following :

[5 x 3 = 15]

2. What is Multiplexer ? Design 4:1 multiplexer using basic logic gates. [5]
3. Distinguish between latch and flip-flop. Write down the difference between combinational and sequential logic circuits. [5]
4. What is the function of comparator in analog to digital converter and write down the applications of analog to digital converter. [5]
5. What do you mean by race around condition and how we can overcome it? [5]
6. Calculate the frequency of 4 bit ripple counter if the time period of last flip-flop is 64 microsecond. [5]

Group-C (Long Answer Type Question)

Answer any three of the following :

[15 x 3 = 45]

7. What do you mean by power amplifier ? What are the different types of power amplifier? Explain the operation of Class B push-pull amplifier? What is crossover distortion? <https://www.makaut.com> [15]
8. Explain the working of a R-2R Ladder type DAC with a neat circuit diagram. [15]
9. Draw and explain Master and Slave JK flip-flop . [15]
10. Design a MOD 8 asynchronous UP/ DOWN counter using JK flip-flop. [15]
11. Why does the dual slope ADC provide excellent noise rejection of AC signal whose periods are integral multiples of the integration time? Find the resolution of a 12 bit DAC converter. What are the advantages and disadvantages of R-2R ladder DAC. [15]

*** END OF PAPER ***