

**CIRCUIT THEORY  
(ELEC 2101)**

**Time Allotted : 3 hrs**

**Full Marks : 70**

***Figures out of the right margin indicate full marks.***

***Candidates are required to answer Group A and  
any 5 (five) from Group B to E, taking at least one from each group.***

***Candidates are required to give answer in their own words as far as practicable.***

**Group – A  
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) Supermesh analysis is based on
    - (a) KCL
    - (b) KVL
    - (c) both KVL & KCL
    - (d) law of conservation of energy
  - (ii) For perfect or ideal coupling, the value of the coefficient of coupling of two magnetically coupled coils is
    - (a) 1
    - (b) 2
    - (c) 0.1
    - (d) 0.2
  - (iii) The Laplace transform of a unit impulse function is
    - (a)  $\frac{1}{s}$
    - (b)  $\frac{1}{s^2}$
    - (c) 1
    - (d) s
  - (iv) Integration of step signal gives
    - (a) Impulse signal
    - (b) Ramp signal
    - (c) Sinusoidal signal
    - (d) Parabolic signal
  - (v) The time constant of an R-L circuit is
    - (a)  $RL$
    - (b)  $\frac{R}{L}$
    - (c)  $\frac{L}{R}$
    - (d)  $L$
  - (vi) A two-port network is symmetrical if and only if
    - (a)  $Z_{11} = Z_{22}$
    - (b)  $BC - AD = -1$
    - (c)  $Y_{12} = -Y_{21}$
    - (d)  $h_{12} = h_{21}$
  - (vii) A network has 8 branches and 5 nodes. The number of fundamental cut-set in the network would be
    - (a) 6
    - (b) 5
    - (c) 4
    - (d) 3
  - (viii) The fundamental cut-set matrix gives the relation between
    - (a) branch voltages and branch currents
    - (b) branch voltages and twig voltages
    - (c) branch currents and link currents
    - (d) link voltages and link currents

- (ix) The transfer function of a normalised 3<sup>rd</sup> order Butterworth low-pass filter is
- (a)  $\frac{1}{(s+1)(s^2+2s+1)}$  (b)  $\frac{1}{(s+1)(s^2+\sqrt{2}s+1)}$
- (c)  $\frac{100}{(s+10)(s^2+10\sqrt{2}s+100)}$  (d)  $\frac{1}{(s+1)(s^2+s+1)}$
- (x) The d.c. gain of a system represented by the transfer function  $\frac{10}{(s+1)(s+2)}$  is
- (a) 1 (b) 2 (c) 5 (d) 10

### Group – B

2. (a) Calculate mesh currents for the circuit of Fig. 2(a).

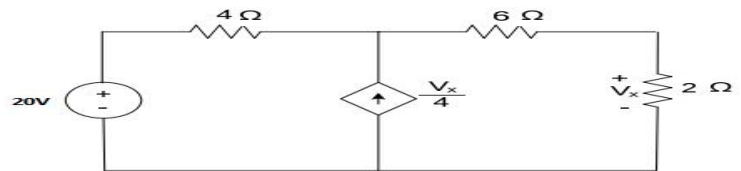


Fig. 2(a)

- (b) Calculate the current through 1Ω resistance using Norton's theorem for the circuit of fig. 2(b).

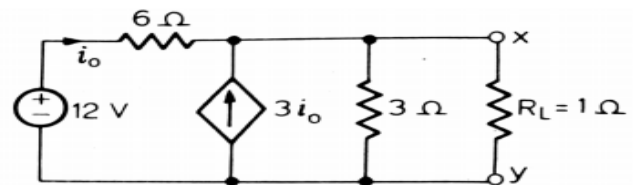


Fig. 2(b)

- (c) In the circuit of fig. 2(c), the load consists of pure resistance  $R_L$ . Calculate the value of  $R_L$  for which the source delivers maximum power to the load.

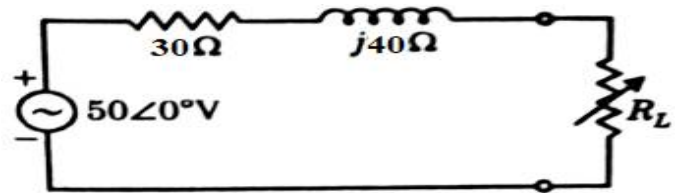


Fig. 2(c)

$$4 + 6 + 2 = 12$$

3. (a) For the circuit shown in fig. 3(a), use superposition theorem to calculate the value of  $i$ .

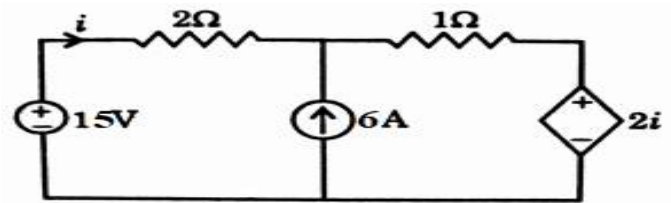


Fig. 3(a)

- (b) Determine the current in 5Ω resistance in the magnetically coupled circuit as shown in fig. 3(b).

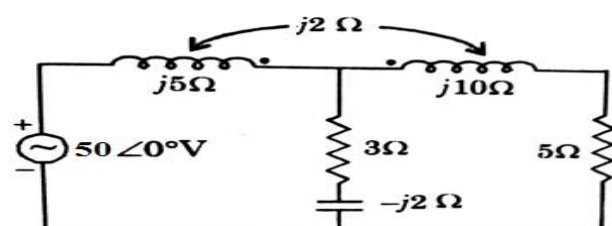


Fig. 3(b)

$$6 + 6 = 12$$

**Group – C**

4. (a) Determine Laplace transform of the waveform shown in fig. 4(a).

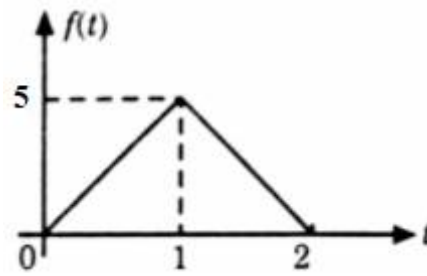


Fig. 4(a)

- (b) In the series R-L-C circuit shown in figure 4(b), the switch S is closed at  $t = 0$ . There is no initial charge on the capacitor. Determine the resulting current for  $t > 0$ . Also determine the nature of damping occurring in the circuit.

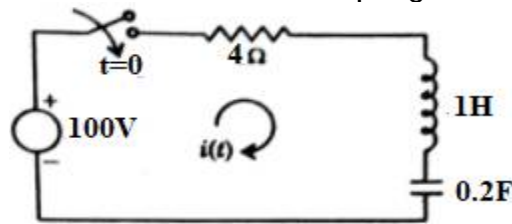


Fig. 4(b)

$$5 + (6 + 1) = 12$$

5. (a) In the network shown in fig. 5(a), the switch 'S' is closed and a steady state is reached in the network. At time  $t = 0$ , the switch is opened. Determine  $i(t)$  for  $t > 0$ .

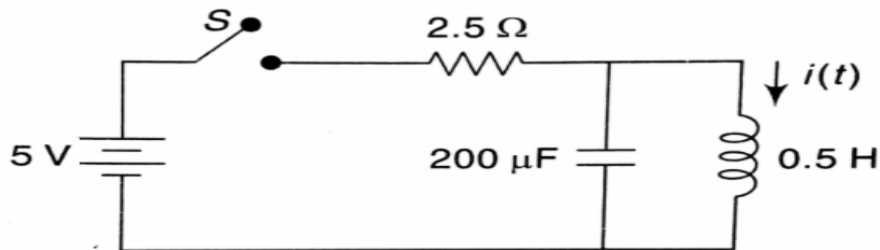


Fig. 5(a)

- (b) Determine the signal  $f(t)$  whose first derivative is as shown in the fig. 5(b). Also sketch waveform of  $f(t)$ .

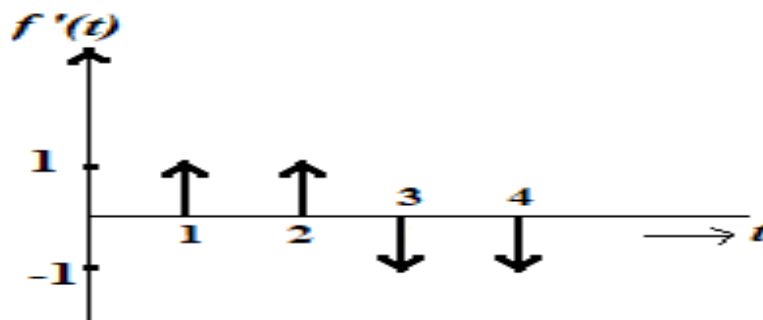


Fig. 5(b)

$$7 + 5 = 12$$

**Group – D**

6. (a) State the properties of Complete Incidence Matrix.

- (b) Draw the oriented graph for the circuit shown in Fig. 6(b). Find its complete incidence matrix and Tie-set matrix. Assume the sub-graph shown in figure below as a tree. Use graph theory to find mesh equations for the circuit.

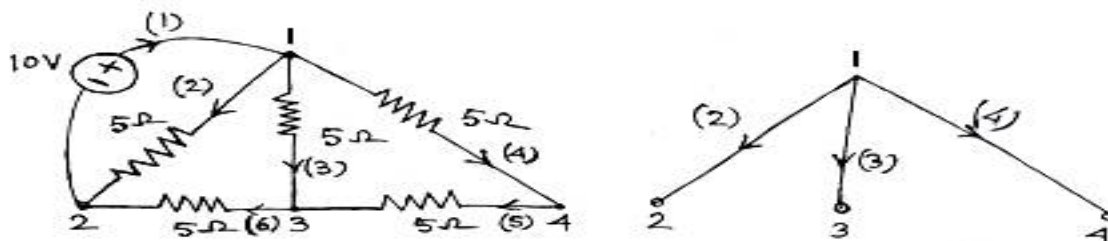


Fig. 6(b)

$$3 + (1 + 2 + 2 + 4) = 12$$

7. (a) Define Z-parameters. Express Z-parameters in terms of Y-parameters and transmission parameters.
- (b) Determine Z-parameters, Y-parameters and ABCD- parameters of the circuit shown in Fig. (7b).

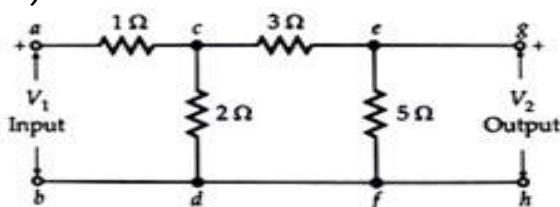


Fig. (7b)

$$(2 + 2 + 2) + (2 + 2 + 2) = 12$$

## Group – E

8. (a) Draw the circuit diagram of a notch filter. Derive the expression transfer function and centre frequency of this filter. Sketch its frequency response curve.
- (b) Design a 2<sup>nd</sup> order Butterworth low pass filter of cut-off frequency 1kHz.
- (1 + 6 + 1 + 1) + 3 = 12
9. Determine the poles of 5<sup>th</sup> order Butterworth filter. Sketch the location of poles on s-plane and hence determine the normalized transfer function of the low pass filter.
- (5 + 3 + 4) = 12

Department & Section	Submission Link
EE regular students	<a href="https://classroom.google.com/c/MTIxOTk2MTM4MTk3/a/MjcxNTUwMTc1NTE2/details">https://classroom.google.com/c/MTIxOTk2MTM4MTk3/a/MjcxNTUwMTc1NTE2/details</a>
EE backlog students	<a href="https://classroom.google.com/c/MjQ4NTI4MDE2NjE4/a/Mjc0MDYyNDI4NTI5/details">https://classroom.google.com/c/MjQ4NTI4MDE2NjE4/a/Mjc0MDYyNDI4NTI5/details</a>