



School of Electronics Engineering
B.Tech. (ECE) -Transmission Lines and Waveguides (ECE2004)
Winter Semester (2017-18) – CAT-I Examination

Faculty Name : Prof.Srinivasarao/ Prof.Poonkuzhali/ Prof.Rajesh/ Prof.Malathi/ Prof.Gopiram/ Prof.Yogesh

Time : 90 Min.

Slot : F1

Marks : 50

Answer ALL the questions.

1. An air filled transmission line has a characteristic impedance of 70Ω and a phase constant of 3 rad/m at 100 MHz . Calculate the inductance per meter and capacitance per meter of the line.

5

2. A 10% voltage drop occurs in 2 km of a uniformly loaded transmission line terminated by its characteristic impedance and there is a phase change of 20° over the same distance at a frequency of 796 Hz . Find the value of line attenuation in dB/km and velocity of propagation.

6

3. Calculate the load impedance of a 50Ω lossless air transmission line of length 2 m , operating at 450 MHz and is connected to an unknown load. The input impedance of the transmission line is $40 + j80 \Omega$.

5

4. If the input impedance of a short and open circuited lossless air transmission line of length 1.5 m are $Z_{sc} = j63 \Omega$, and $Z_{oc} = -j75 \Omega$ respectively, determine the characteristic impedance Z_0 and propagation constant of the line.

4

5. A 75Ω lossless transmission line of electrical length $l = 0.3\lambda$ is terminated with a complex load impedance $Z_L = 30 - j25 \Omega$. Find the reflection coefficient at the load, the SWR on the line, the reflection coefficient at the input of the line, and the input impedance to the line.

10

6. Prove that a $\lambda/2$ open circuit transmission line will act like a parallel resonator and determine R, L, C and Quality factor of the resonator.

10

7. Consider the transmission line circuit shown below. Compute the incident power, reflected power, and the power transmitted into the infinite 100Ω line.

10

