



KEEPING MOBILE PHONE/SMART WATCH, EVEN IN 'OFF' POSITION, IS EXAM MALPRACTICE

Answer ALL Questions

(i) How the diode will behave when a small low frequency signal and high frequency signal are applied to it? Draw the ac equivalent circuit for the two cases mentioned in the question. [10]

(ii) A PN junction operating in the forward-bias region with a current I of 1 mA is found to have a diffusion capacitance of 10pF. What diffusion capacitance do you expect this junction to have at $I = 1\text{mA}$? What is the mean transit time for this junction?

[OR]

1. b) Derive the expression for voltage gain (A_M) and upper cutoff frequency f_H using hybrid π model of BJT with a neat diagram. [10]

Given $I_C = 0.8\text{ mA}$, $R_1 = 68\text{ K}\Omega$, $R_2 = 27\text{ K}\Omega$, $R_C = 4.7\text{ K}\Omega$, $R_E = 2.2\text{ K}\Omega$, $R_{sig} = 10\text{ K}\Omega$, $R_L = 10\text{ K}\Omega$, $\beta_0 = 200$, $C_\mu = 0.8\text{ pF}$, $f_T = 1\text{ GHz}$. Neglect the effect of r_x and r_o . Find the midband gain and upper-3dB frequency of the CE amplifier. Also calculate the value of R_L that reduce the midband gain to half the value, and hence find the upper-3dB frequency of the CE amplifier for the reduced gain. [10]

3. Find the C_{C1} , C_{C2} and C_S for a CS amplifier for which $R_G = 4.7\text{ M}\Omega$, $R_D = R_L = 5\text{ k}\Omega$, $R_{sig} = 100\text{ k}\Omega$, $r_o = 70\text{ }\Omega$ and $g_m = 1\text{ mA}$. It is required to have f_L at 100Hz. [10]

4. For a N-channel MOSFET with $t_{ox} = 25\text{ nm}$, $L = 2\text{ }\mu\text{m}$; $W = 20\text{ }\mu\text{m}$, $L_{ov} = 0.07\text{ }\mu\text{m}$, $V_o = 0.55\text{ V}$, $C_{sbo} = C_{dbo} = 15\text{ fF}$, $V_{SB} = 1.2\text{ V}$ and $V_{DS} = 2.5\text{ V}$. Determine a) Oxide capacitance, b) Overlap capacitance, c) Gate-Source capacitance, d) Gate-Drain capacitance, e) Source-Bulk capacitance and f) Drain-Bulk capacitance. [10]

5. a) The class-A amplifier shown in Fig.1 is biased at $V_{CE} = 12\text{ V}$. The output voltage is the maximum possible without distortion. Find [10]

- the average power from the dc supply,
- the average power delivered to the load,
- the efficiency,
- Draw the transfer characteristics of the amplifier showing the load lines and locate the Q-point.

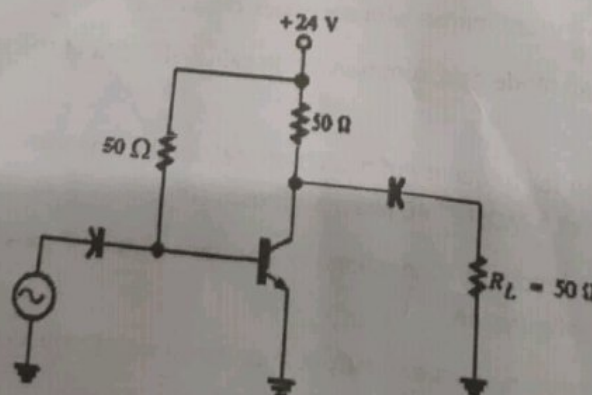


Fig.1

[OR]

5. b) For an PMOS differential pair with a common-mode voltage V_{CM} applied, as shown in Fig.2., let $V_{DD} = V_{SS} = 2.5$ V, $k'_n W/L = 3$ mA/V², $V_{th} = 0.7$ V, $I = 0.2$ mA, $R_D = 2$ k Ω , and neglect channel-length modulation. [10]
- Find V_{OV} and V_{GS} for each transistor.
 - For $V_{CM} = 0$, find v_{s1} , i_{D1} , i_{D2} , V_{D1} , and V_{D2} .
 - Repeat (b) for $V_{CM} = +1$ V.
 - Repeat (b) for $V_{CM} = -1$ V.
 - What is the highest value of V_{CM} for which Q_1 and Q_2 remain in saturation?

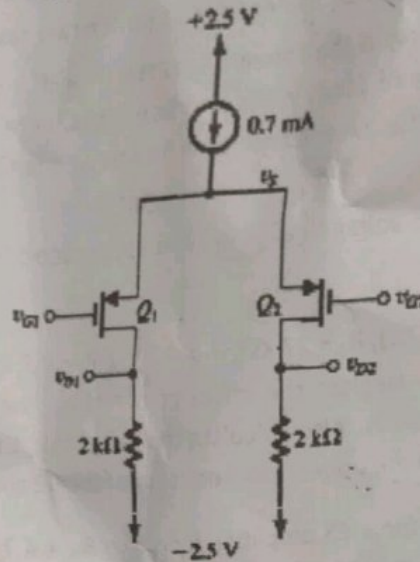


Fig.2

At an instance, consider a class B amplifier provides a 10 V peak signal to a 4 Ω load and a power supply of 12 V, [10]

- Determine the input power, output power and efficiency of the amplifier.
- What will be the peak output voltage when the class B amplifier provides efficiency of 78.54%?
- Compute the maximum input power, maximum output power and maximum efficiency of the amplifier.
- Estimate the maximum power dissipated by each transistors of the amplifier.

7. Explain Wilson MOS current mirrors with necessary circuit diagrams. [5]

8. Derive the differential mode gain, common mode gain and CMRR of the MOS differential pair, with neat sketch. [10]

9. Derive the expression for frequency of oscillation, gain of the amplifier and feedback gain to obtain sustained oscillation of a MOSFET RC phase shift oscillator. [10]

10. Explain the effect of feedback connection on input and output impedance for voltage series and voltage shunt and configuration. [5]

11. Determine the voltage gain, input and output impedance with feedback for voltage series feedback having $A = -100$, $R_i = 10$ k Ω and $R_o = 20$ k Ω for feedback of $\beta = -0.5$. [5]

12. Explain the recent trends and techniques used in analog electronic circuits. [5]



2 Vcc