

भारतीय सूचना प्रौद्योगिकी संस्थान कोटा
INDIAN INSTITUTE OF INFORMATION TECHNOLOGY KOTA

B.Tech. (ECE), Semester – IV
End Term Examination, Even Semester 2023-24

Measurement and Instrumentation Technology (ECT204)

Marks: 40 (Weightage – 40%)

Time: 120 minutes

Date: May 14, 2024

Note: Attempt all questions in sequence.

Q1. Answer in brief.

[2×11 = 22 Marks]

- i. Name different components of a measurement system.
- ii. Express the following derived units in terms of base SI units: Farad, Ohm.
- iii. Mention at least four classification of instruments based on type and method of measurements.
- iv. Define standards and calibration.
- v. Mention the percentage of values that lie within a band around the mean in a normal distribution curve with a width of two and four times of standard deviations, respectively.
- vi. Two resistors, with given nominal values \pm uncertainty, R_1 ($100 \pm 0.1 \Omega$) and R_2 ($50 \pm 0.03 \Omega$) are connected in series and then in parallel. Calculate equivalent resistance (nominal value \pm resulting uncertainty) for series and parallel connections.
- vii. Derive the expression of gage factor for a strain gage with circular cross-section.
- viii. Consider a full-bridge circuit having identical strain gages with nominal resistance equal to 130Ω . If each strain gage cannot sustain power dissipation of more than 0.35 W , what is the maximum value of the input excitation?
- ix. With the help of schematic diagram, explain the working principle of LVDT.
- x. Design an active band-reject filter with following specifications: band-pass gain = 2 V/V , lower cut-off frequency = 100 Hz , upper cut-off frequency = 1000 Hz . Use OPAMP ICs 741, capacitors with $1 \mu\text{F}$ and resistors of appropriate values.
- xi. A pressure sensor outputs a voltage varying as 100 mV/psi and has $2.5 \text{ k}\Omega$ output impedance. Design an OPAMP based signal conditioning circuit to provide 0 to 2.5 V as the pressure varies from 50 to 150 psi .

Q2. A piezoelectric transducer having a capacitance of 1000 pF and charge sensitivity of $40 \times 10^{-3} \text{ coulomb/cm}$ is connected to a CRO having resistance of $1 \text{ M}\Omega$ in parallel with 50 pF by a cable which has a capacitance of 300 pF .

- i. Find the sensitivity of the transducer alone in V/cm .
- ii. Find the overall sensitivity of the system in V/cm .
- iii. Find the time-constant of the system.
- iv. Find the maximum operating frequency in rad/sec so that the amplitude-ratio error is no worse than 5% .

[1+1+1+3 = 6 Marks]

Q3. Two ideal op-amps are used to linearize the output of a single active arm Wheatstone bridge, shown in **Figure 1**. The resistance of the variable resistor is given by $R_v = R + \Delta R$, where $\Delta R > -R$.

- Find an algebraic expression for $V_o = f(V_s, R, R_1, R_2)$.
- Let $V_s = 5\text{ V}$, $R = R_1 = R_2 = 1\text{ k}\Omega$. Find the permissible range in R_v so that neither op-amp's output reaches $\pm 12\text{ V}$ (saturation). [3+3 = 6 Marks]

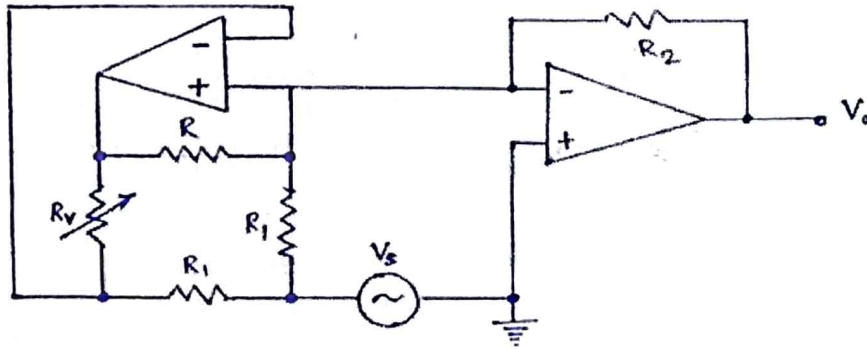


Figure 1

Q4. Consider a rectangular strip of gold sample with length L , width W , and thickness D ($1\text{ }\mu\text{m}$) as shown in **Figure 2**. A current I (100 mA) is passed along L , perpendicular to the cross-sectional area $W \times D$. The face $W \times L$ is exposed to a magnetic field intensity B . A voltmeter is connected across the width to read the Hall voltage V_H . What is the magnetic field that can be recorded per micro-volt of Hall voltage?

Given: density of gold is 19.32 g/cm^3 ; $1\text{ gm-atomic weight of gold (196.97 gm)}$ contains atoms 6.0225×10^{23} (Avogadro number); gold is monovalent, meaning each atom contributes one conduction electrons. [6 Marks]

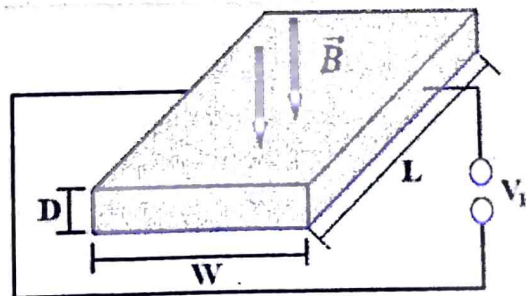


Figure 2

*** Be Good, Do Good ***