



Programme Name & Branch: B.Tech.

Course Code & Name: MEE1037, Automotive Electronics

Class Number: VL2019201002022

Slot: E1+TE1

Exam Duration: 90 Mins.

Maximum Marks: 50

Faulty Name: Dr. Ravi Verma

General instruction(s): Missing data, if any, may be suitable assumed.

Answer all the questions


(5 x 10 = 50 Marks)

1. Design the circuit diagram of full adder and full subtractor.

$$(A \oplus B) C$$
$$AB + BC + AC$$
$$\bar{A}B + B\bar{C} + \bar{A}C$$

2. Explain about the different types on interrupts in microprocessor?

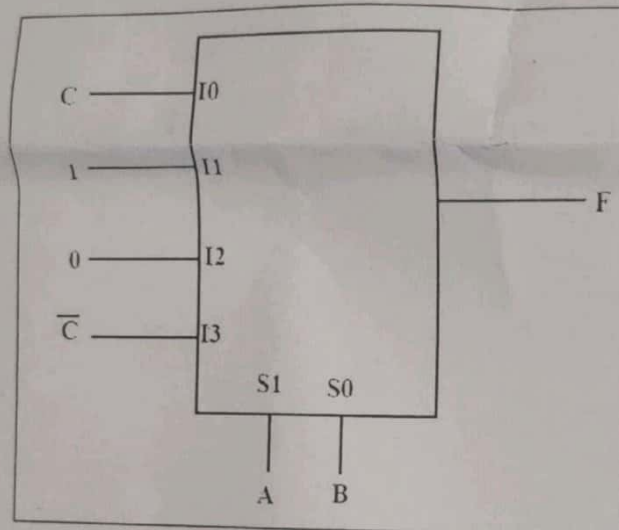3. Find the minimize expression for the multiplexer shown below?



$$B\bar{C} + \bar{A}C$$

4. Minimize the expression using K-Map,

$$F(A, B, C, D) = \sum m(0, 1, 4, 5, 8, 9, 13, 15).$$

$$\bar{A}\bar{C} + \bar{B}\bar{C} + ABD$$

5. Design the circuit diagram and write truth table, excitation table, characteristics equation of SR flip flop, JK flip flop, D flip flop and T flip flop.

SR JK