
 


2.3 Schottky diode hot carrier diode

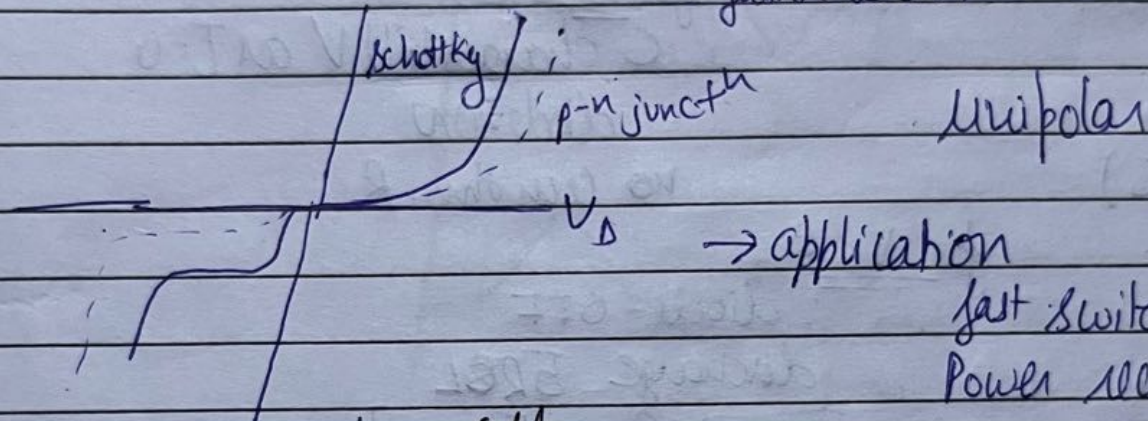

- Construction (metal instead of p-type)
- Working (no minority carrier, only e^- , high kinetic negative wall)




- application
- fast switching
- Power rectifier
- Solar cell
- LED

2.4 Zener & avalanche breakdown diff

2.5 Clipper & Clamper

Answer

 

Ruhanika105

506 answers • 550.2K people helped

Since there are no minority carriers in the junction, the 'storage' time (the time required for the minority carriers to recombine with the majority carriers in the junction) is zero.


The only time required for the diode to turn off is the transit time of the majority carriers across the junction.

Thus schottky diode helps in reducing storage time.

hope it helps....



quarterfreelp and 2 more users found this answer helpful


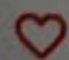
 **THANKS 2**

 **0.0** (0 votes)




[Log in](#) to add comment

mod-1 (Prev Year)

  

for the half cycle

 

(a) when $V_i < V$

D_1 will be O.C. (O.C.)

open circuit

output will follow input

(b) when $V_i > V$

replace D_1 with 0V (ideal)

$$V_o = V_i - V$$

for -ve half

input = output

(b)

What is Gray Code?

This code belongs to a class of codes called minimum change code in which only one bit in the code group changes when going from one step to the next.

This is an un-weighted code which means that there are no specific weights assigned to the bit positions. Because of this the **Gray code** is not suited for arithmetic operations but finds applications in input/output devices and some types of analog to digital converters (ADCs).

Advantages of Gray Code

In Gray code, if we go from one decimal number to next, only one bit of the gray code changes. Because of this feature, an amount of switching is minimized and the reliability of the switching systems is improved.

Advantage of grey code over binary is only one-bit changes for each step. This will be useful in circuits that are sensitive to glitches. Example: When you use grey code to trim the output impedance of IO blocks, there won't be a huge jump in codes momentarily that would cause reflection.

The reflected binary code was originally designed to prevent spurious output from electromechanical switches. Today, Gray codes are widely used to facilitate error correction in digital communications such as digital terrestrial television and some cable TV systems.

2

3

4

5

Category

> C Program


> What is &

> Advantag

Full Subtractor using NAND


$$diff = A \oplus B \oplus C$$
 
$$borrow = A\bar{B} + B\bar{C}_{in} \quad (A \oplus B)$$



→ CMRR

 Common mode rejection ratio
It is the ratio of differential mode voltage
gain (A_d) to common mode voltage



→ CMRR

Common mode rejection ratio
It is the ratio of differential mode voltage gain (A_d) to common mode voltage gain

$$CMRR = \frac{A_d}{A_c}$$

Ideally $CMRR = \infty$
 $A_c = 0$

Numerical

$$A_c = 0.2$$

$$CMRR = 3250$$

Ans = 4.55 V
rms

$$CMRR = \frac{A_d}{A_c}$$

$$A_d = 0.2 \times 3250 = 650$$

$$V_o = A_d V_d$$

$$A_d = \frac{V_o}{V_d}$$

Good Write

$$650 \times 7 \text{ mV} = 4.55 \text{ V}$$



$$4550 \text{ mV} = 4.55 \text{ V rms}$$

Ques $F(A, B, C, D) = \sum (0, 2, 3, 4, 6, 12) + d(8, 10, 11, 14)$

CD \ AB	00	01	11	10
00	0	1	0	0
01	0	5	7	6
11	0	3	15	X
10	X	9	X	X

Pos

$$F = D \cdot (B + \bar{C})$$

  

Ans I_{CBO} and I_{CEO}

→ I_{CBO} & I_{CEO}
↓


Both of these are leakage currents

I_{CBO} → current flows through collector base in reverse bias when emitter is open circuit
(Happens in common base)

I_{CEO} → current that flows through collector emitter in reverse bias when base is open circuited
(Happens in common emitter)

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \quad |_{I_B = 0}$$

Common emitter

 

stability factor

- Temp
- ① I_{CO}
 - ② β
 - ③ V_{BE}

- ① Saturation
- ② Cutoff
- ③ Center

$$I_{CEO} = (1 + \beta) I_{CBO}$$

$$I_C = I_{EO} + \beta I_B$$

V_{BE} changes $2.5 \text{ V/}^\circ\text{C}$

β_{DC} varies with temp so I_C also varies
as $I_C = \beta I_B$

Stabilization - process of making operatⁿ
pt independent of change
in temp changes or
variation

Thermal Runaway

Flow of collector current and
also the collector leakage current
cause heat dissipatⁿ in unstabilized
circuit which leads to self
destruction

I_C inc

$P = 12 \text{ W}$

Stabilizat

I_{CBO}

β_{DC}


V_{BE}

Voltage divider biasing

It is preferred over other
biasing as it gives complete
control over current &

voltage each component
receives in the transistors.

 Also R_E helps stabilize the
value of β gain despite fluctuation
in β



$$I_{DSS} = 9 \text{ mA}$$

$$V_p = -4.5 \text{ V}$$

$$r_d = 40 \text{ k}\Omega$$

Z_i, Z_o, A_v

$$Z_i = R_G$$

$$Z_o = r_d \parallel R_S \parallel 1/g_m$$

$$A_v = \frac{v_o}{v_i} = \frac{g_m(r_d \parallel R_S)}{1 + g_m(r_d \parallel R_S)}$$

$$Z_i = R_G = 10 \text{ M}\Omega$$

$$Z_o = 40 \parallel 2.2 \parallel \frac{1}{2.28}$$

$$g_m = -\frac{2 I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p}\right)$$

$$A_v = \frac{v_o}{v_i} = \frac{g_m(r_d \parallel R_S)}{1 + g_m(r_d \parallel R_S)}$$


Good Write

$$\frac{V_A}{R_i} = -\frac{V_O}{R_f} \quad V_O = 1 + \frac{R_f}{R_i}$$

$$\frac{V_O}{V_{in}} = -\frac{R_f}{R_i}$$

DATE: ___/___/___
PAGE: ___

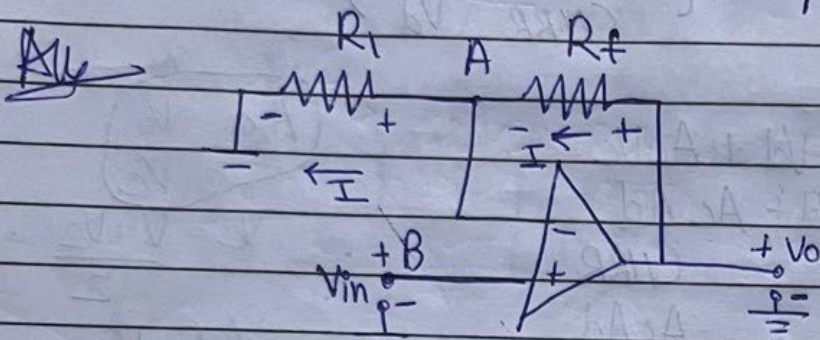Ques. Draw circuit diagram of closed loop non-inverting op-amp and derive the expression for its voltage gain. Locate virtual ground point in circuit & explain its significance.



from eq - (1) & (2)

$$\frac{V_O - V_{in}}{R_f} = \frac{V_{in}}{R_i}$$

$$\frac{V_O}{R_f} = \frac{V_{in}}{R_i} + \frac{V_{in}}{R_f}$$

$$\frac{V_O}{R_f} = \frac{V_{in} (R_i + R_f)}{R_i R_f}$$

$$A_{VF} = \frac{V_O}{V_{in}} = \frac{(R_i + R_f) R_f}{R_i R_f}$$

$$= \frac{R_i + R_f}{R_i} = 1 + \frac{R_f}{R_i}$$

$$V_A = V_B = V_{in}$$

from output side

$$I = \frac{V_O - V_A}{R_f}$$

$$I = \frac{V_O - V_{in}}{R_f} \quad \text{--- (1)}$$

at inverting terminal

$$I = \frac{V_A - 0}{R_i}$$

$$I = \frac{V_{in}}{R_i} \quad \text{--- (2)}$$

Practical op amp


- ① very high vol gain
- ② " " input impedance
- ③ very low output "
- ④ wide bandwidth

~~Don't~~ Calculating virtual ground


$$I = \frac{V_O}{R_f} \quad \text{--- (1)}$$

$$I = \frac{V_{in}}{R_i} \quad \text{--- (2)}$$

→ Common Source JFET

 

low frequency ac. circuit

 

$$Z_i = R_G \parallel R_1 \parallel R_2$$

$$Z_o = R_D \parallel R_S \parallel 1/g_m$$

$$A_v = \frac{V_o}{V_i} \quad V_o = I_d (R_D \parallel R_S)$$

putting eqn $I_d = -g_m V_{gs}$

$$V_o = -g_m V_{gs} (R_D \parallel R_S)$$

$$A_v = \frac{g_m (R_D \parallel R_S)}{1 + g_m (R_D \parallel R_S)}$$

$$V_{in} = -V_{gs} + V_o$$

$$0 = -V_{gs} (1 + g_m (R_D \parallel R_S))$$