



General Instruction: Important constants: $k = 1.38 \times 10^{-23} \text{ J/K}$, $h = 6.625 \times 10^{-34} \text{ J-s}$, $m_e = 9.11 \times 10^{-31} \text{ kg}$, $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/cm}$, $q = 1.6 \times 10^{-19} \text{ C}$, For Si: $E_g = 1.12 \text{ eV}$, $n_i (300 \text{ K}) = 10^{10} / \text{cm}^3$, $\epsilon_r = 11.7 \epsilon_0$

Answer ALL Questions
(10 X 10 = 100 Marks)

- a) i) A thin film of silicon layer was grown using chemical vapour deposition. It was found that the doping concentrations $N_A = 5 \times 10^{17} \text{ cm}^{-3}$ and $N_D = 3 \times 10^{15} \text{ cm}^{-3}$ at 300 K. Find the following:
- Type of semiconductor
 - Position of Fermi-level from valance band at equilibrium.
 - Minority carrier concentration
- ii) A Si bar was doped with boron at 10^{15} cm^{-3} . A short pulse of light was exposed and found the electron-hole pair generation rate as $10^{20} / \text{s-cm}^3$ and recombination lifetime as $10 \text{ } \mu\text{s}$. Determine the following:
- Majority and minority carrier concentrations
 - Excess charge carriers produced after illumination of light

[OR]

- b) In a 5.4 mm long n-type silicon bar with rectangular cross section $50 \text{ } \mu\text{m} \times 100 \text{ } \mu\text{m}$, the measured drift current at 300 K was $2.8 \text{ } \mu\text{A}$. It was found that the electron mobility is $1500 \text{ cm}^2/\text{V-s}$ for the donor concentration is $5 \times 10^{18} / \text{cm}^3$. Assume $\mu_p = 450 \text{ cm}^2/\text{V-s}$. Calculate:

- Electron and hole concentrations
- Resistivity of the sample.
- Average electric field across the sample

Applied voltage across the sample.

2. A p-n junction has a built-in potential of 0.65 V and the donor concentration on the N-side is 5 times the acceptor concentration on the P-side. If the intrinsic carrier concentration is 10^{11} cm^{-3} at 100°C , find the doping concentration on the P-side, width of the depletion region and the distance it extends in the P-side and in the N-side of the junction. Also, find the value of the depletion capacitance when a reverse bias of 2 V is applied across it for a cross sectional area of 0.5 cm^2 . Assume the relative dielectric constant is 10.

3. With the help of band diagrams explain the operation and V-I characteristics of tunnel diodes.

4. Explain the differences between Avalanche and Zener breakdown mechanisms.

5. Analyze the circuit (by determining V_D & v_o). Assume circuit and diode parameters of $V_{DS} = 5 \text{ V}$, $R = 5 \text{ k}\Omega$, $V_f = 0.6 \text{ V}$ & $v_i = 0.1 \sin \omega t$.

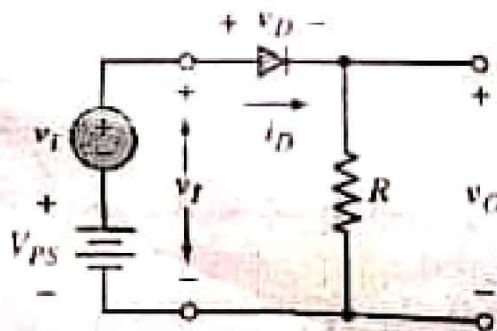


Fig.1



2024
VIT QUESTION PAPERS
ON TELEGRAM



Possession of Mobile Phone in the exam hall even in switched off condition is a malpractice.

5. a) Determine the output waveform of the given circuit.

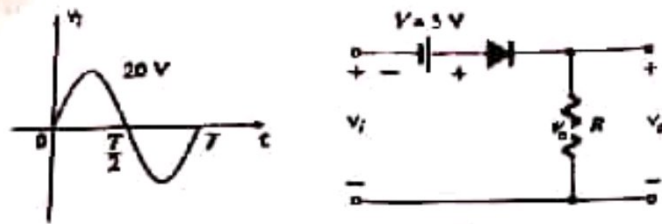


Fig.2

- b) (i) Sketch the output v_o and determine the dc level of the output for the network, Fig.3
 (ii) Repeat part (a) if the ideal diode is replaced by a silicon diode.
 (iii) Repeat parts (a) and (b) if V_m is increased to 200 V and compare solutions.

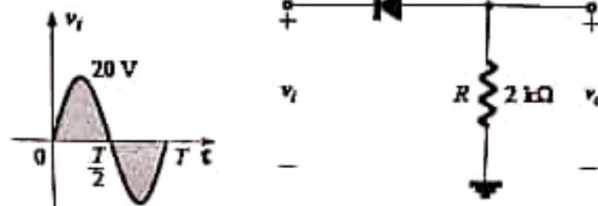


Fig.3

6. a) Determine the V_o for the circuit. (Fig.4)

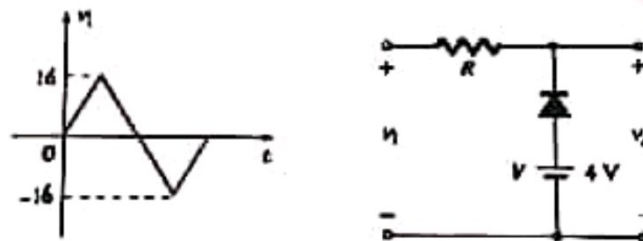


Fig.4

b) Determine the output waveform for the network and calculate the output dc level and the required PIV of each diode.

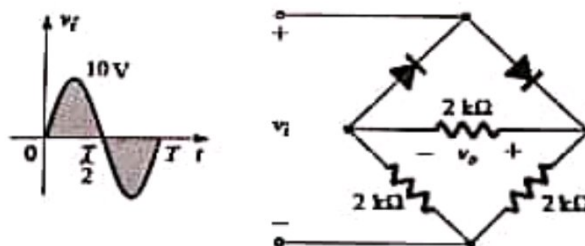


Fig.5

7

Determine Q point, I_{CQ} and V_{CEQ} . Assume $\beta_{DC} = 200$ and $V_{BE} = 0.7V$.

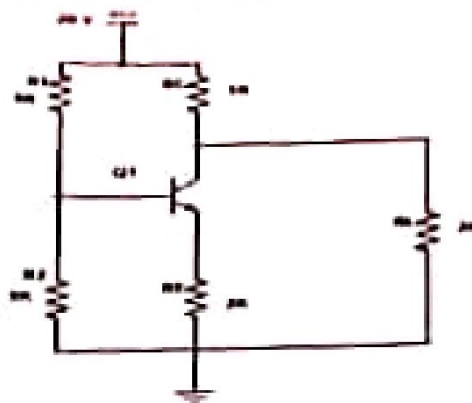


Fig. 6

Find the values of voltages at emitter, collector and base terminal and the current flowing through each terminal. Use $\beta = 30$ and $V_{BE} = 0.7V$.

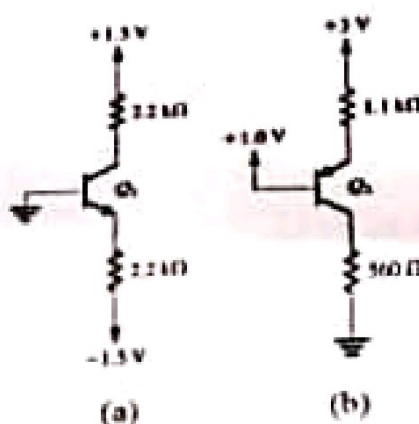


Fig. 7

9. a) i) Calculate the total charge in the channel of NMOS Transistor which has:

$$C_{ox} = 9 \frac{fF}{\mu m^2}; L = 0.36 \mu m; W = 3.6 \mu m; V_{GS} = 0.2V \text{ and } V_{DS} = 0V.$$

ii) Refer to the Fig. 8 the MOSFET has $V_t = 0.7V$; $\mu_n C_{ox} = 100 \mu A/V^2$; $L = 1 \mu m$ and $W = 32 \mu m$. Design the circuit to have a drain current of $0.4mA$ with $V_D = +0.5V$, calculate the values of R_S and R_D .

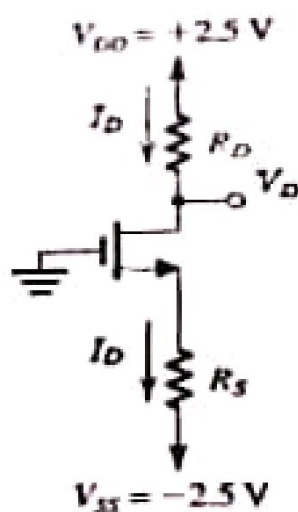


Fig. 8

(20)

- 8) The NMOS and PMOS transistors in the circuit in Fig 9 are matched with $k_n'(W_L/L_D) = k_p'(W_P/L_P) = 1 \text{ mA/V}^2$ and $V_{TN} = -V_{TP} = 1 \text{ V}$. Assuming $\lambda = 0$ for both the devices, find the drain currents i_{DSN} and i_{DSP} and the voltage v_o for $v_i = 0 \text{ V}$, $+2.5 \text{ V}$ and -2.5 V .

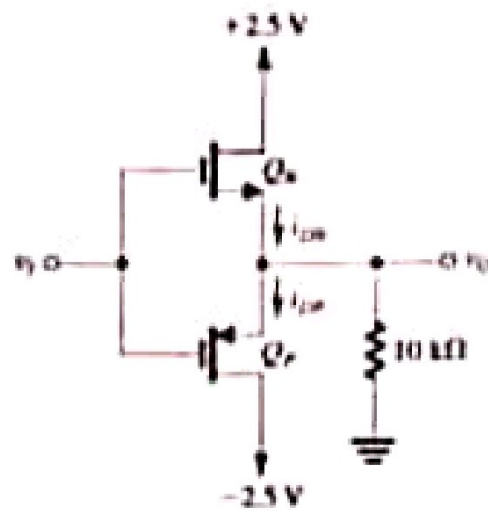


Fig 9

10.

Determine the dc transistor currents and voltages in a circuit in Fig 10 containing an enhancement load device. The transistors in the circuit (shown in Figure) have parameters $V_{TN} = V_{TP} = 1 \text{ V}$, $k_{n0} = 50 \mu\text{A/V}^2$, and $k_{p0} = 10 \mu\text{A/V}^2$. Also assume $I_{D0} = I_{L0} = 0$. (The subscript D applies to the driver transistor and the subscript L applies to the load transistor.) Determine V_{DS} for $V_i = 5 \text{ V}$ and $V_i = 1.5 \text{ V}$.

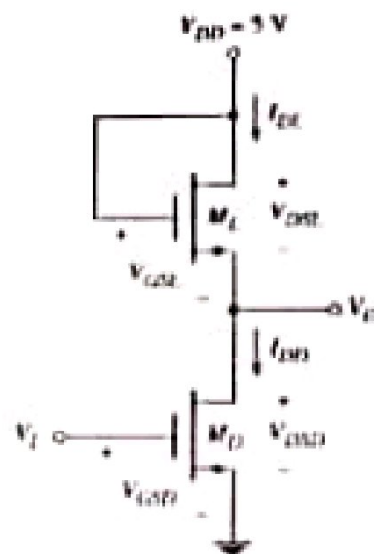


Fig 10

CSCS