

ODD SEMESTER EXAMINATION, 2024 – 25



2nd Year (III Sem) B.Tech.: Electronics & Communication Engineering

Networks & Systems


Duration: 3:00 hrs

Max Marks: 100

Note: - Attempt all questions. All Questions carry equal marks. In case of any ambiguity or missing data, the same may be assumed and state the assumption made in the answer.

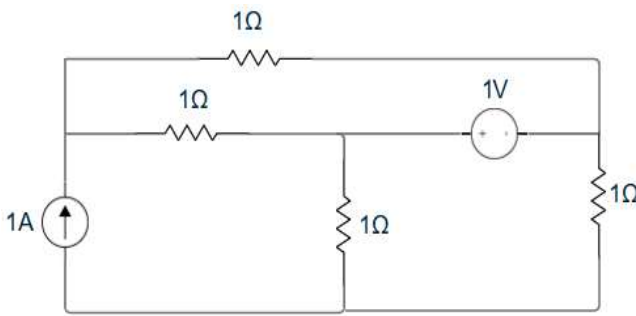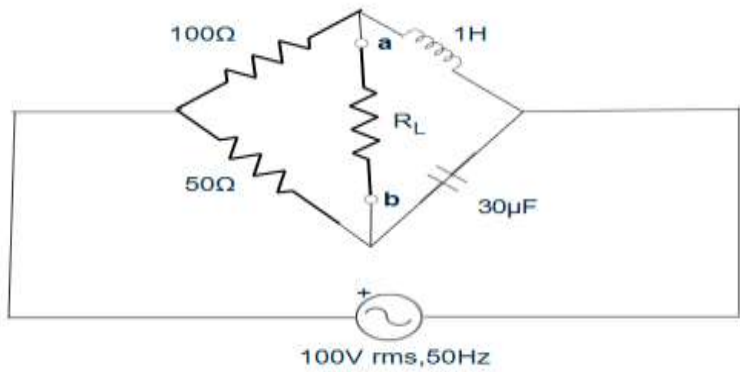
Q 1.	<p>Answer any two parts of the following. (10x2= 20)</p> <p>a) (i) What are independent and dependent sources? What are unit step, unit ramp & unit impulse signals. (5 marks)</p> <p>(ii).What are the different circuit elements. Explain each one of them. (5 marks)</p> <p>b) Describe any five properties of linear- time invariant system. (10 marks)</p> <p>c) Find power by dependent sources (i.e. I & V source). (10 marks)</p> 
Q 2.	<p>Answer any two parts of the following. (10x2= 20)</p> <p>a) (i) What are the properties of a tree in the graph theory. What is the relationship between twigs and links. (5 marks)</p> <p>(ii) Derive the expression for the maximum power delivered to the load resistor R_L in terms of the source voltage V_s and the internal resistance R_s. (5 marks)</p> <p>b) Find thevenin equivalent across R_L i.e. ab. (10 marks)</p> 

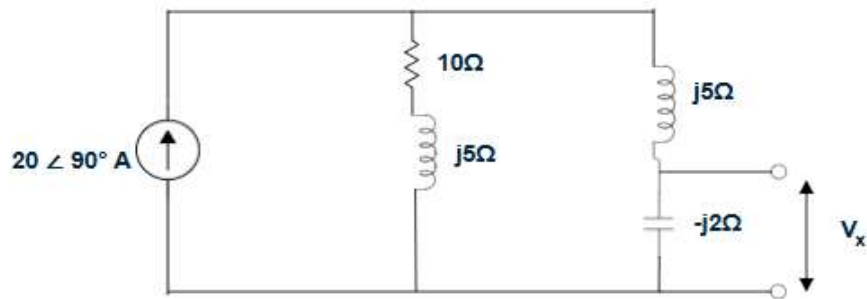c) Determine the voltage V_x , then apply reciprocity theorem and compare the two voltages. (10 marks)




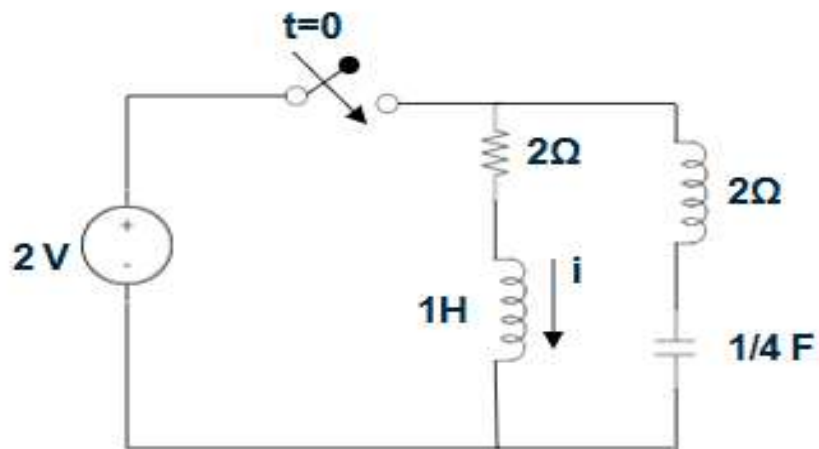Q 3. Answer any two parts of the following. (10x2= 20)


- Define and derive the general expression for the Fourier series of a periodic signal. (5 marks)
 - State and explain the major properties of the Fourier series (e.g., linearity, time-shifting, frequency-shifting, etc.). (5 marks)
- Using Laplace transform, find the solution for the current $i(t)$ in an RL series circuit with a step input voltage $V(t)=V_0$. Find expression for current $i(t)$, if switch is opened at $t=0$. (10 marks)



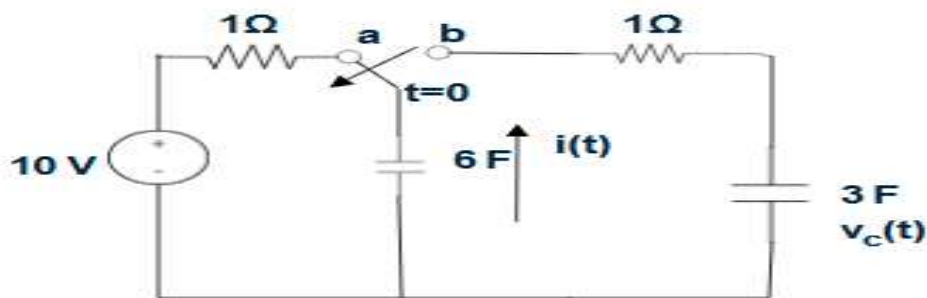c) The switch in the circuit is in position **a** for long time and then moved to position **b** at time $t = 0$. Find current $i(t)$ using Laplace Transform. (10 marks)



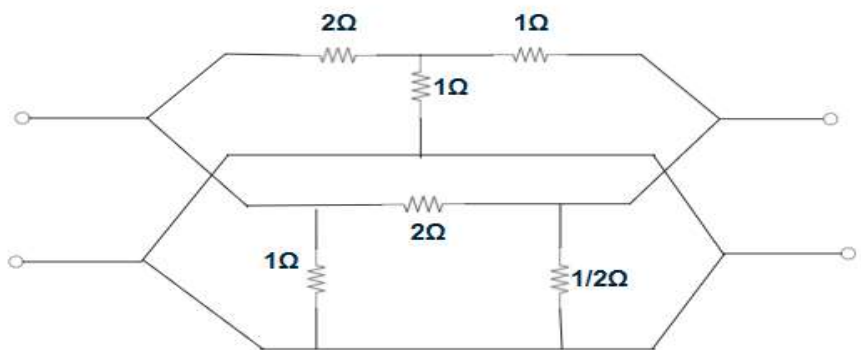- Q 4. Answer any two parts of the following. (10x2= 20)
- a) (i) What are ladder networks and lattice networks? How are they constructed using two-port networks? (5marks)
- (ii) Draw the equivalent circuit of a two-port network using h-parameters. (5 marks)
- b) Derive the condition of Reciprocity and Symmetry for T parameters. (10 marks)
- c) Find Y parameters? (10 marks)



- Q 5. Answer any two parts of the following. (10x2= 20)
- a) (i) Define the network function of a two-terminal network and explain how impedance & admittance functions are derived. (5 marks)
- (ii) Discuss the relationship between the transfer function and impulse response of a system. How are poles and zeros related to the transfer function? (5 marks)
- b) Find the Cauer I and II forms of the RL impedance function (10 marks)
- $$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$
- c) Find Foster I and II forms (10 marks)
- $$Z(s) = \frac{(s+1)(s+3)}{(s+2)(s+4)}$$
