



Name :

Roll No. :

Invigilator's Signature :

**CS/B.TECH (IT) OLD /SEM-3/EC-311/2012-13
2012**

ELECTRONIC SYSTEM DESIGN

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for the following :

10 × 1 = 10

- i) An operational amplifier is a direct coupled
 - a) high gain amplifier
 - b) low gain amplifier
 - c) very high gain amplifier.
- ii) An operational amplifier consisting of
 - a) one differential amplifier
 - b) two differential amplifier
 - c) one or more differential amplifier.

3253 (O)

[Turn over



- iii) Digital ICs are
 - a) Flat pack type
 - b) Metal cane type
 - c) DIP.
- iv) Linear ICs require
 - a) positive supply voltages
 - b) negative supply voltages
 - c) both positive and negative supply voltages.
- v) Digital ICs require
 - a) positive supply voltages
 - b) negative supply voltages
 - c) both positive and negative supply voltages.
- vi) An ideal Op-Amp has
 - a) finite slew rate
 - b) infinite slew rate
 - c) zero slew rate.
- vii) The use of negative feedback in a non-inverting amplifier
 - a) increase the input impedance
 - b) decrease the input impedance
 - c) increase the output impedance.



- viii) The order of the filter indicates rate at which
- out put changes
 - input changes
 - none of these.
- ix) The window detector uses
- one comparator and one two threshold levels
 - two comparator and two threshold levels
 - two comparator and one threshold levels.
- x) Astable multivibrator has
- one stable and one quasi-stable state
 - two stable states
 - two quasi-stable states.

GROUP – B

(Short Answer Type Questions)

Answer the following questions.

3 × 5 = 15

- Define
 - input offset voltage
 - input offset current
 - input bias current
 - out put resistance
 - CMRR.
- Design an amplifier to obtain $V_0 = V_1 + 3V_2 + \frac{1}{3} V_3$.
- Draw a circuit diagram of astable multivibrator using IC555 and explain its operations. Derive the expression for free running frequency.



GROUP – C

(Long Answer Type Questions)

Answer the following questions.

3 × 15 = 45

5. a) Draw the circuit diagram of a Logarithmic Amplifier and derive the equation for output voltage.
b) What do you mean by instrumentation amplifier ? Draw the circuit diagram of a basic instrumentation amplifier and derive the expression for output voltage.
6. Draw the a.c. equivalent circuit of a dual input balanced output amplifier. Find out the gain, input and output resistance.
7. Write short notes on any *three* of the following : 3 × 5
 - a) V-F Converter
 - b) Window Detector
 - c) Precision Rectifier
 - d) Schmitt Trigger
 - e) F-V Converter.

=====