

**VIT**

Vellore Institute of Technology

Final Assessment Test – June 2023

Course: BEEE102L - Basic Electrical and Electronics Engineering

Class NBR(s):4570


Slot: A1+TA1

Time: Three Hours


Max. Marks: 100

KEEPING MOBILE PHONE/SMART WATCH, EVEN IN 'OFF' POSITION IS TREATED AS EXAM MALPRACTICE**General Instructions: Assume suitable data if required.****Answer any FIVE Questions****(5 X 20 = 100 Marks)**

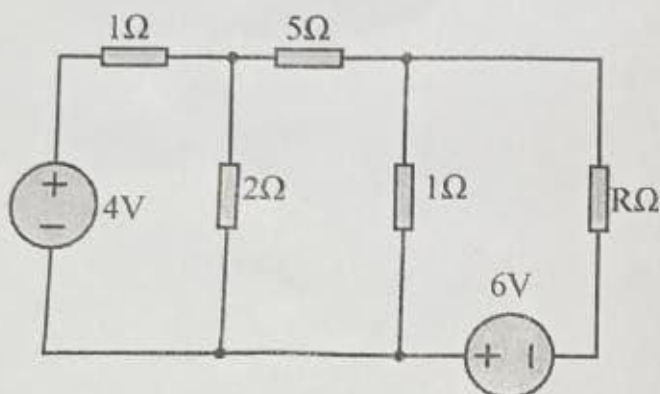1. a) Apply maximum power transfer theorem to calculate maximum power [10]
transferred through the load ($R\Omega$) for the circuit given below.



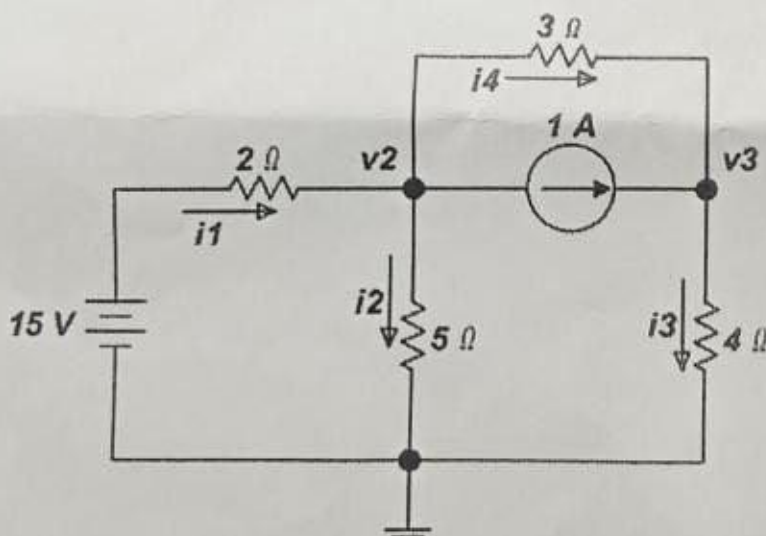- b) Calculate node voltages (v_2 and v_3) and branch currents (i_1 , i_2 , i_3 and i_4) [10]
currents for the circuit given below.



2. a) A 240 V, 50 Hz AC supply is applied to a coil of 0.08 H inductance and 4 Ω [10]
resistance connected in series with a capacitor of 8 μF . Calculate the following
(i) Impedance, (ii) Circuit current, (iii) Phase angle between voltage and current,
(iv) Power factor (v) Power consumed, and (vi) Q-factor of the circuit at resonant
frequency. Draw phasor diagram of the circuit.
- b) Three identical coils, each of resistance 10 Ω and inductance 42mH are [10]
connected (a) in star and (b) in delta to a 415V, 50 Hz, 3-phase supply.
Determine the total power dissipated in each case.