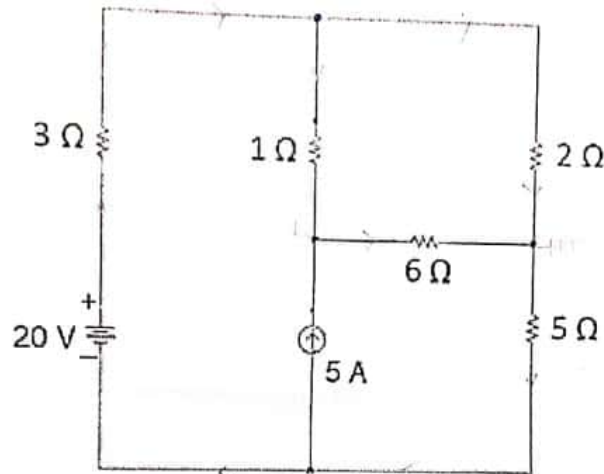





Answer any **TEN** Questions  
(10 X 10 = 100 Marks)

1. Using nodal analysis, find the current through  $6\ \Omega$  resistor in the circuit given in Fig below

SEARCH VIT QUESTION PAPERS  
ON TELEGRAM TO JOIN



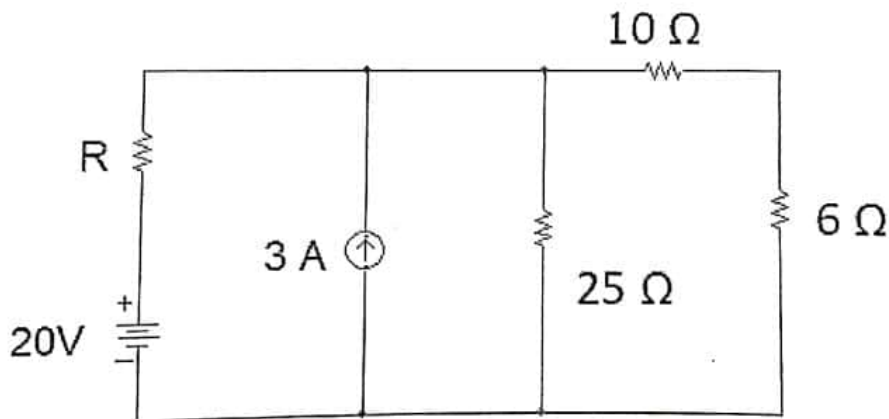2. For the circuit shown in Fig below, find the value of unknown resistance "R" so that maximum power will be transferred to load. Calculate the maximum power



3. A series circuit having a resistance of  $40\ \Omega$ , inductance of  $50.07\text{mH}$  and a capacitor is connected across a  $400\text{V}$ ,  $50\text{Hz}$ , AC Supply. This RLC combination draws a current of  $10\text{A}$ . Calculate (i) Power factor (ii) Capacitor value (iii) Real and reactive power
4. A series combination of  $3\ \Omega$  resistance and a  $796.18\ \mu\text{F}$  capacitor in each branch forms a three phase star connected balanced load which is connected to a  $415\text{V}$ , 3 phase,  $50\ \text{Hz}$ , AC supply. Calculate (i) Current drawn by the load (ii) Power consumed. If the same load is now connected as delta, calculate (iii) Current drawn by the load (iv) Power consumed. Give your inference on the power consumed in both the cases.



5. Simplify the expression  $F(W, X, Y, Z) = \sum (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$  using K-map. Draw the logical circuit for the simplified expression.

6. a) From the truth table, derive the logic circuit for a full adder using half adder circuits.

[7]

b) Convert the following into binary

[3]

$108.125_{10}$

$AB.CD_{16}$

$77.177_8$


7. With necessary diagrams, explain the construction and principle of operation of a DC motor. List out its classification.

8. Explain the operation of a transformer with relevant diagrams. Derive the emf equation of a transformer.

9. With relevant diagrams, explain the operation of Regulated Power Supply. Draw the output voltage waveform of each component.

10. With necessary graphs and diagrams, explain the input and output characteristics of an NPN transistor in CE configuration

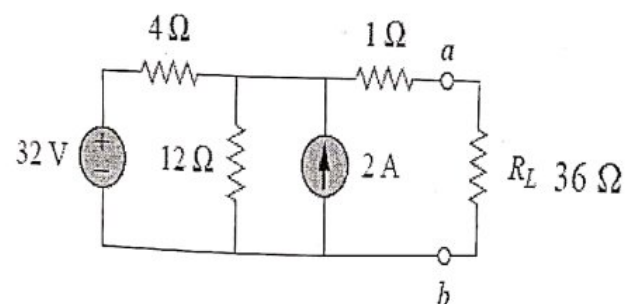11. Using Thevenin's theorem, find the current through the load resistance  $R_L$



12. A series RC circuit is connected across 200V, 50 Hz ac supply draws a current of 20A. When the frequency of the supply is 100Hz, the current increases to 23.4082A. Calculate the value of resistance and capacitance of the circuit.

