



MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY, WEST BENGAL

Paper Code : PE-EE 601B HVDC Transmission

UPID : 006746

Time Allotted : 3 Hours

Full Marks : 70

The Figures in the margin indicate full marks.

Candidate are required to give their answers in their own words as far as practicable

Group-A (Very Short Answer Type Question)

1. Answer any ten of the following :

[1 x 10 = 10]

- (I) Mention the Types of filters.
- (II) What are the requirements of a good simulation tool?
- (III) State the advantages of parity simulator.
- (IV) What are the approaches used for transient analysis of electrical network?
- (V) List the types of power devices for HVDC transmission.
- (VI) What is meant by pulse number of a converter?
- (VII) How can the converter configuration defined?
- (VIII) How power is reversed in HVDC link?
- (IX) What is radio interference?
- (X) What are the application of HVDC transmission?
- (XI) What is LASCR? How does it differ from a conventional SCR?
- (XII) Mention the various modes of operation of inverter characteristics.

Group-B (Short Answer Type Question)

Answer any three of the following :

[5 x 3 = 15]

2. Draw and explain the circuit of Graetz circuit. [5]
3. Draw and explain the circuit diagram of 12 pulse converter. [5]
4. What are the importance of the firing angle of the converter valve? [5]
5. Mention and explain the various modes of operation of rectifier characteristics. [5]
6. Compare insulation characteristics of DC and AC cable. [5]

Group-C (Long Answer Type Question)

Answer any three of the following :

[15 x 3 = 45]

7. (a) What is the need for interconnection of systems? Explain the merits of connecting HVAC systems by HVDC tie-lines. [8]
- (b) With the help of a neat schematic diagram of a typical HVDC converter station, explain the functions of various components available. [7]
8. (a) Discuss the effect of pulse number and overlap angle on harmonics generated by HVDC converters. [8]
- (b) Using fourier analysis show that the lowest order voltage harmonic present in Graetz circuit output voltage is six. [7]
9. (a) What is the reason for using star-star and star-delta transformer configurations for 12 pulse converter? Derive an equation for primary current using fourier analysis. [10]
- (b) Clearly explain how harmonics are produced and obtain the expression for rms value of the fundamental component of the current, [5]
10. (a) Explain with neat sketch, constant extinction angle control. [9]
- (b) What is meant by current margin between two stations in a HVDC link? [6]
11. (a) Explain the drawbacks in Individual phase control and equidistant pulse control schemes used in HVDC projects. [7]
- (b) Write short notes on the (a) Constant Alpha control and (b) Inverse cosine control. [8]

*** END OF PAPER ***