

Code No: 151AG

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B. Tech I Year I Semester Examinations, March/April - 2023****BASIC ELECTRICAL ENGINEERING****(Common to EEE, CSE, IT, CSIT, ITE, CE(SE), CSE(CS), CSE(DS), CSE(N), CSD)****Time: 3 Hours****Max. Marks: 75****Note:** i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, Answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART – A**(25 Marks)**

- 1.a) State Norton's Theorem. [2]
- b) Write short notes on voltage source and current source. [3]
- c) Define power factor. What is the ideal value of power factor? [2]
- d) What is balanced system and unbalanced system? [3]
- e) Write the applications of an auto transformer. [2]
- f) What is meant by ideal transformer? What are the properties of ideal transformer? [3]
- g) Write the applications of single-phase induction motor? [2]
- h) A 3 phase 4 pole, 50 Hz induction motor is running at 1455 rpm. Find the slip speed and slip. [3]
- i) What is the component used in L.T switch gear. [2]
- j) Define earthing, explain its importance? [3]

PART - B**(50 Marks)**

- 2.a) Using Thevenin's theorem, calculate Thevenin's Resistance, Thevenin's voltage across 5 ohms resistor (figure 1).

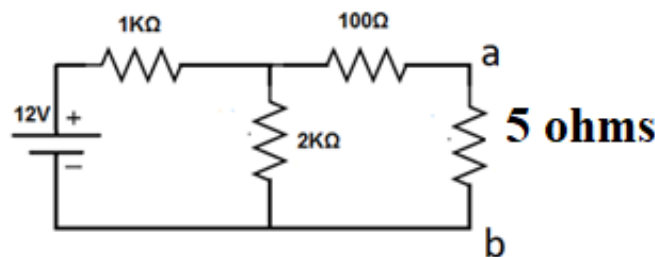


Figure 1

- b) Find the current 'i' in the circuit below figure 2.

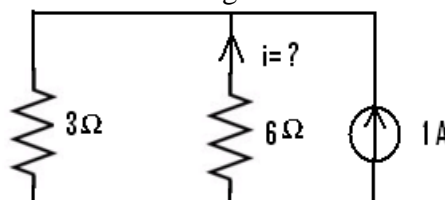
[6+4]

Figure 2

OR

- 3.a) State and explain Superposition Theorem.
b) Define time constant. Explain the time domain analysis of first order Series RL circuit. [5+5]

- 4.a) Find the impedance of series R-L-C circuit with $R=50\Omega$, $X_L=25\Omega$ and $X_C=10\Omega$.
b) Derive the average value, peak value, form factor for a sine waveform. [4+6]

OR

- 5.a) Derive an expression for average power in a single-phase circuit contains L element across sinusoidal voltage.
b) Give the relationship between phase voltage and line Voltage, phase current and line current for balanced three phase delta connected system. [5+5]

- 6.a) What are the various connections of three phase transformer?
b) Define voltage regulation, what is the meaning of zero regulation in transformer? [6+4]

OR

- 7.a) Explain types of losses that takes place in a transformer.
b) Draw and explain the equivalent circuit of a transformer. [5+5]

- 8.a) Explain the constructional details of three phase induction motor.
b) Draw torque slip characteristics of three phase induction motor. [5+5]

OR

- 9.a) Explain the constructional details of synchronous generator.
b) What are different methods to control speed of induction motor? [5+5]

- 10.a) Explain the types of batteries and its important characteristics.
b) Mention the importance of power factor improvement. [5+5]

OR

- 11.a) Write a short notes on battery back-up.
b) Explain how an MCB Works. [5+5]

---ooOoo---