



General Instructions: n_i for Ge = $2.5 \times 10^{13} \text{ cm}^{-3}$, n_i for GaAs = $2 \times 10^6 \text{ cm}^{-3}$

Answer ALL Questions
(10 X 10 = 100 Marks)

1. Calculate the position of the Fermi level and sketch its band diagram for the following cases: [10]

- Ge, n-type, $N_D = 10^{17} \text{ cm}^{-3}$, $T = 300 \text{ K}$.
- Si, p-type, $N_A = 2 \times 10^{18} \text{ cm}^{-3}$, $T = 450 \text{ K}$.
- GaAs, n-type, $N_D = 10^{18} \text{ cm}^{-3}$, $N_A = 5 \times 10^{17} \text{ cm}^{-3}$, $T = 300 \text{ K}$.

2.(a) A Si p-n junction is reverse-biased with $V_a = -10 \text{ V}$, $N_D = 2 \times 10^{15} \text{ cm}^{-3}$ and $N_A = 2 \times 10^{16} \text{ cm}^{-3}$. Determine the percentage change in junction (depletion) capacitance and built-in potential if the doping in the p region is increased by a factor of 2. [10]

OR

2.(b) A Si p-n junction has $N_D = 10^{18} \text{ cm}^{-3}$ and $N_A = 10^{16} \text{ cm}^{-3}$. The junction area is $100 \mu\text{m}^2$. Calculate the junction (depletion) capacitance in the absence of any applied bias. [10]

3. Sketch the transfer characteristic for the circuit shown in fig.1 with the input range of $-20 \text{ V} \leq V_1 \leq 20 \text{ V}$. Case (i) Assume the diodes are ideal. (ii) Suppose diode D2 is reversed in the circuit. [10]

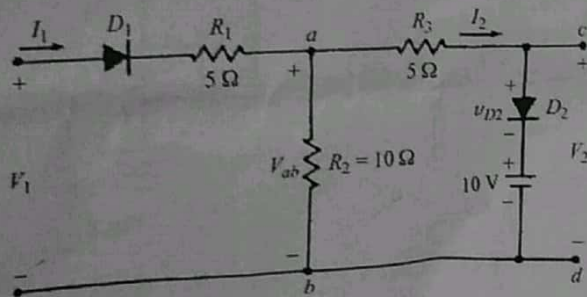


Fig.1

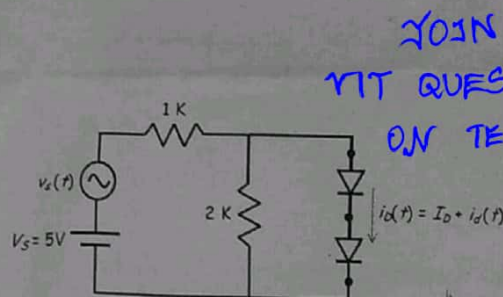


Fig.2

For the circuit shown in Fig. 2, if $v_s(t) = 0.01 \sin \omega t$, $\eta = 1$ and $V_T = 0.6 \text{ V}$ what is $i_o(t)$? [10]

4. Determine the average voltage and current, rms voltage and current and ripple factor for the filtered bridge rectifier with a load as indicated in Fig.3. [10]

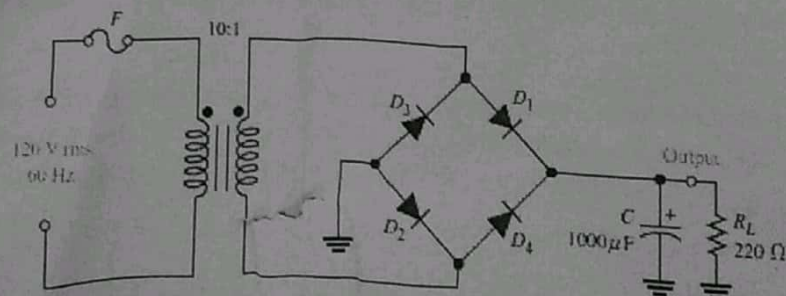


Fig.3

Discuss in detail about the different regions of operation of Enhancement MOSFET and the various modes of operation of a BJT along with their I-V Characteristics. [10]

- A Ge transistor with $\beta = 100$ has a base-to-collector leakage current I_{CBO} of $5 \mu\text{A}$. If the transistor is connected for common-emitter operation, find the collector current for (i) $I_B = 0$ and (ii) $I_B = 40 \mu\text{A}$. [5]
- The Si transistor in Fig. 4 has $\alpha = 0.99$ and $I_{CEO} = 0$. Also, $V_{EE} = 4 \text{ V}$ and $V_{CC} = 12 \text{ V}$. (i) If $I_{EQ} = 1.1 \text{ mA}$, find R_E . (ii) If $V_{CEQ} = -7 \text{ V}$, find R_C . [5]

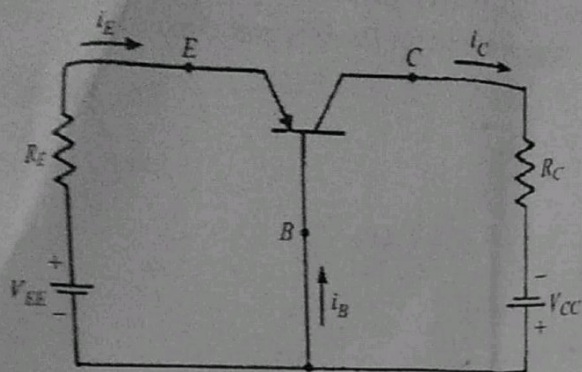


Fig.4

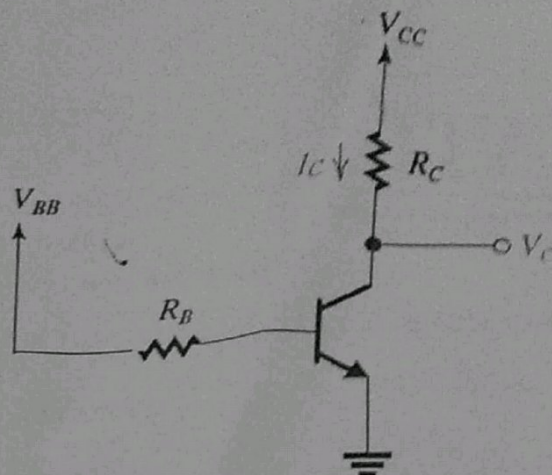


Fig.5

8. Find the value of V_{BB} for the circuit shown in fig.5 with $V_{CC} = 5\text{ V}$, $R_C = 1\text{ k}\Omega$, $\beta = 50$ and $R_B = 20\text{ k}\Omega$ that results in the transistor operating (a) in the active mode with $V_C = 1\text{ V}$; (b) at the edge of saturation; (c) deep in saturation with $\beta_{forced} = 10$ [10]

9. Find I_{D2} and V_{D2} for the circuit shown in Fig.6. Consider that $V_t = 0.6\text{ V}$, $\mu_n C_{ox} = 200\text{ }\mu\text{A/V}^2$, $L = 0.8\text{ }\mu\text{m}$, $W = 8\text{ }\mu\text{m}$, $R_{D1} = 12.5\text{ k}\Omega$, $R_{D2} = 10\text{ k}\Omega$, $V_{DD} = 3\text{ V}$. Assume that Q1 and Q2 are identical. [10]

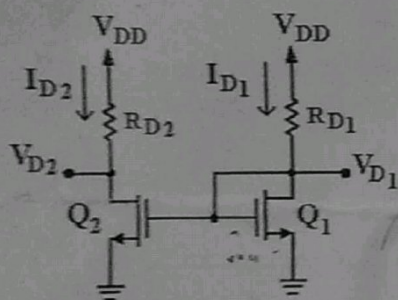


Fig.6

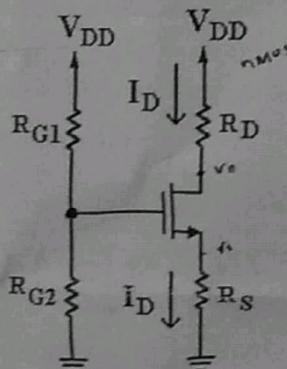


Fig.7

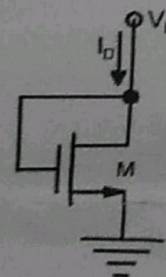


Fig.8

- 10.(a) For the circuit shown in Fig.7, assume that the NMOS transistor has $V_{TH} = 1\text{ V}$, $k'_n (W/L) = 1\text{ mA/V}^2$, and $R_{G1} = R_{G2} = 10\text{ M}\Omega$, $R_D = R_S = 6\text{ k}\Omega$, and $V_{DD} = 10\text{ V}$. [10]

- Determine the voltages at all nodes and the currents through all branches.
- What is the largest value that R_D can have while the transistor remains in the saturation mode?

OR

- 10.(b) i) Find the small-signal resistance (i.e. dV_B/dI_D) in $\text{k}\Omega$ offered by the n-channel MOSFET 'M' shown in Fig. 8, at a bias point of $V_B = 2\text{ V}$ is (device data for M: device transconductance parameter $k_N = \mu_n C_{ox} \frac{W}{L} = 40 \frac{\mu\text{A}}{\text{V}^2}$, threshold voltage $V_{TH} = 1\text{ V}$, and neglect body effect and channel length modulation effects). [5]

- For the two circuits shown in Figure 9(a) and 9(b), Plot I_x as V_x varies from 0 to 3 V. The technology parameters $k'_N = \mu_n C_{ox} \approx 100 \frac{\mu\text{A}}{\text{V}^2}$ ($W/L = 10$, $V_t = 0.7\text{ V}$).

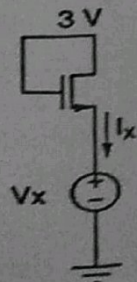


Fig.9 (a)

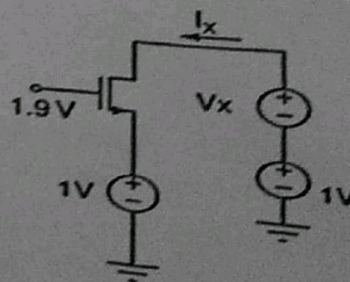


Fig.9 (b)