

<b>SLOT: B2+TB2</b>			
School of Information Technology and Engineering			
Winter Semester 2022-2023		Continuous Assessment Test – I	
Programme Name & Branch		B.Tech. Information Technology	
Course Code:	BEEE102L	Course Title:	Basic Electrical and Electronics Engineering
Class Number(s)	VL2022230500372; VL2022230505828		
Faculty Name(s)	Arun S L; Rajesh Kumar Lenka		

**Exam Duration: 90 Min.**

**Maximum Marks: 50**


**General instruction(s): Answer all questions.**

**Q.No.**

**Question**


**Max  
Marks  
10**

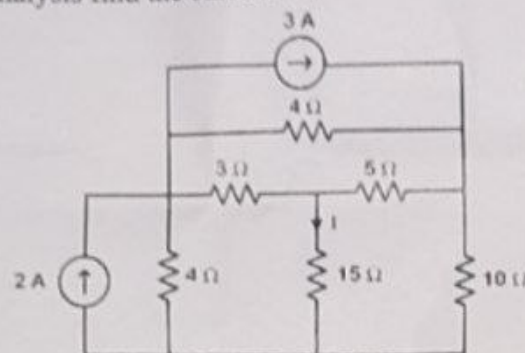1. Using nodal voltage analysis find the current 'I'.



2. When the load resistance ( $R_L$ ) is equal to  $5\Omega$ , it absorbs maximum power. Find the value of resistance  $R_S$  and also compute the maximum power absorbed by load resistance.

10

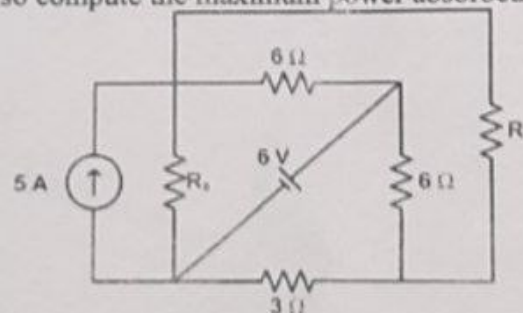

3. Using superposition theorem find the current 'i'.

10

