

2nd Semester B.Tech. Mid Term Examination 2019-2020

BASIC ELECTRICAL ENGINEERING(18ESIT02)

Duration: 01:30

Full Marks: 25

1 Answer All

- a Mark the correct option from the following choices. 1

For a series RC circuit excited by a dc voltage V_0 , the initial current is:

- (a) zero (b) infinity
(c) V_0/R (d) V_0/C

- b What is the power consumption for a purely capacitive circuit? 1

2 Answer any Two


- a What is the difference between Thevenin's theorem and Norton's theorem? 2
- b How will you prove that efficiency under maximum power transfer conditions is 50%? 2
- c Three resistances of 3 ohms each are connected in delta. What is the value of the resistance in equivalent star? 2

3 Answer any Two


- a What is an impedance triangle? Draw the impedance triangle for a series R-L circuit and series R-C circuit. 2
- b A 125V ac source supplies a series circuit consisting of a $20.5\mu\text{F}$ capacitor and a coil whose resistance and inductance are 1.06Ω and 25.4mH , respectively. The source frequency is adjusted so as to bring the circuit to resonance. Determine source frequency. 2
- c A current of 10A flows in a circuit lagging behind the applied voltage of 100V, 50Hz, by 30° . Determine the value of resistance, reactance, and impedance of the circuit. 2

4 Answer any Two

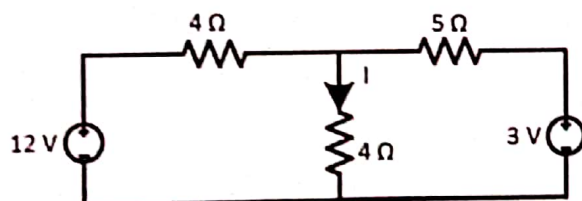- a State and explain the maximum power transfer Theorem with an example. 5
- b Find the current I using superposition theorem. 5



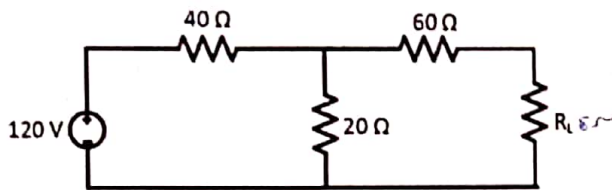- c Find the value of load resistance R_L for maximum power transfer. Also, determine the maximum power. 5



5 Answer any One

- a State the condition for resonance to occur in a series R-L-C a.c circuit and derive an expression for the resonant frequency. Also, draw the resonance curve and explain its properties. 5
- b An Impedance $Z_a = (2 + j3)\Omega$ is connected in parallel with another impedance $Z_b = (1 - j2)\Omega$. If the input reactive power is 100 VAR, what is the total active power? 5
