



MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY, WEST BENGAL

Paper Code : PE-EE 601B HVDC Transmission

UPID : 006746

Time Allotted : 3 Hours

Full Marks : 70

The Figures in the margin indicate full marks.

Candidate are required to give their answers in their own words as far as practicable

Group-A (Very Short Answer Type Question)

1. Answer *any ten* of the following :

[1 x 10 = 10]

- (I) What is meant by an Asynchronous tie?
- (II) Define current margin.
- (III) What are two types of programs used for HVDC system studies?
- (IV) What are the types of DC link?
- (V) List different types of converters in HVDC systems.
- (VI) What is the necessity of control in a DC link?
- (VII) State the ill effects of harmonics injected into the AC line?
- (VIII) Write equations representing the equivalent circuit of lumped element.
- (IX) What is meant by pulse number of a converter?
- (X) What are advantages of EMPT representation of elements in DC system?
- (XI) Why circuit turn off time should be greater than the thyristor turn-off time?
- (XII) Mention the various modes of operation of rectifier characteristics.

Group-B (Short Answer Type Question)

Answer *any three* of the following :

[5 x 3 = 15]

2. Explain protection of converter station against over current and over voltages. [5]
3. Briefly state the effect caused by harmonics. [5]
4. Explain drawbacks of constant current control (CCC). [5]
5. Compare insulation characteristics of DC and AC cable. [5]
6. Explain the criteria for selection of DC filter. [5]

Group-C (Long Answer Type Question)

Answer *any three* of the following :

[15 x 3 = 45]

7. (a) Differentiate between the two start-up procedures based upon the pulse. [8]
(b) Describe starting and stopping of DC link. [7]
8. (a) Explain in detail, the different configurations of static VAR system. [6]
(b) Derive an equation for harmonic voltage and current for single tuned filter and discuss the influence of network admittance on design. [9]
9. (a) Explain the characteristics of a Rectifier and an Inverter with sketches. [9]
(b) With a block diagram, discuss the principle of operation of a basic power controller. [6]
10. (a) What are the various sources of harmonics generation in a HVDC line? [5]
(b) Derive the relationship between pulse conversion and harmonics generated. [5]
(c) What are the affects of Harmonics produced by the HVDC converters? [5]
11. For a 3- Φ , 6 pulse Graetz's circuit, draw the timing diagram considering overlap angle is less than 60° and without overlap for the following: [15]
(a) Voltage across load
(b) Voltage across any two pair of conduction valves

*** END OF PAPER ***