## Minor

## Course Title: Digital Circuit System

**Duration: 2:00 Hours** 

MM: 30

Note:

1. All parts of a question should be answered consecutively.

2. Question paper has three sections and all the sections are compulsory.


10x1=10SECTION A

(1) Design astable/bistable multivibrator using one XOR and two NOT gates.

(2) Using BJT (Transistor), design logic circuit for following Boolean expression.

 $Y=(A+B)C+\overline{D}$ 

 
(3) For the logic circuit shown in the figure below, the required input condition (A, B, C) to make output (X) = 1.



(4) Implement  $Y = A\overline{B}C$  using minimum number of 2-input NAND gates.

(5) Convert (48)10 into Excess-3 code.

 (6) The figure shows the internal schematic of a TTL AND-OR inverter (AOI) gate. For the input shown in the figure the output Y is.




(7) Given  $X = (1101010)_2$  and  $Y = (0101011)_2$ , (a) find X-Y and (b) find Y-X using 2's complements. (8) Minimize the logical Boolean expression  $Z = (X, \overline{Y}) + (\overline{X}, Y)$  into reduced form.


(9) In a number system with radix "r", the decimal value of (110), is equal to 12. Calculate the decimal

(10) Subtract (3A5)16 from (592)16. Wing 2's 10 m plement

 (1) For the given digital circuits draw the timing diagram and calculate the duration of glitch. [5]



 (2) Map 3-variable K-MAP into 4-variable K-MAP. Also design logic circuit using minimum number of logic gates. [5]




(3) For the given K-map, find Implicant, Prime Implicant, Essential Prime Implicant, Redundant Prime Implicant, and Selective Prime Implicant. Also give the reduced Boolean expression and its logic circuit. [5]

1		1
1		1
1		
1	1	1

## **SECTION C**

 (1) Design a full adder from truth table and draw the timing diagram at following given inputs. Also calculate max (Tsum, Tcarry) for given propogation delay of gates (AND = 10 ns, XOR = 30 ns, and OR = 20 ns) and carry input delay is 10 ns. [5]



(2) Design a two-bit (inputs) comparator with output A=B, A>B, and A<B for given variables A&B. Use AND-OR logic to design circuit. [5]

(3) Given  $F(w,x,y,z) = \Sigma(0,1,2,3,7,8,10) + \Sigma d(5,6,11,15)$ . What is the minimum POS form of OR F(w,x,y,z)? Further, design a logical circuit using resistor and BJT. [5]