



JOIN  
VIT QUESTION PAPERS  
ON TELEGRAM



**VIT**  
Vellore Institute of Technology  
Established in 1984 by Sri. R. V. S. Murthy, Founder Chairman, VIT


## School of Electronics Engineering

Continuous Assessment Test – II | ECE1002 – Semiconductor Devices and Circuits  
Class Number: VL2018195001226, 1229, 1232, 1234, 1236, 1240, 1248

Slot: C2+TC2


Maximum Marks: 50 Marks

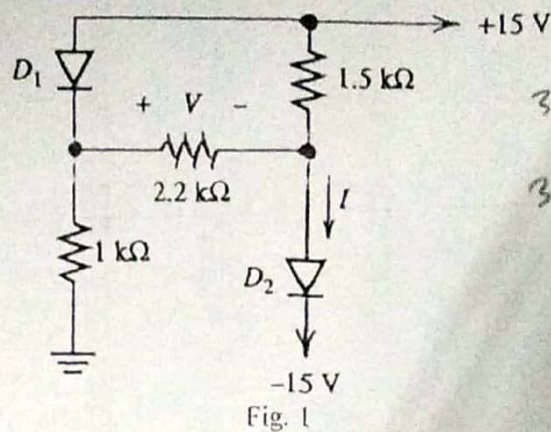- Determine the values of current ( $I$ ) and voltage ( $V$ ) for the circuit shown in Fig. 1. [10]  
Assume the diodes are ideal
  - Repeat (a) considering the diodes are silicon.



336 mA  
30V

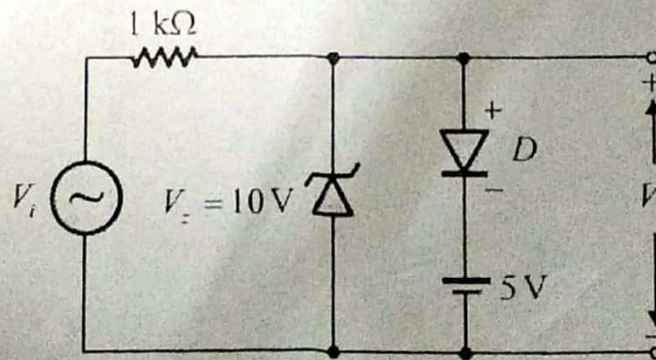- Sketch the transfer characteristic curve for the circuit shown in Fig. 2. Assume the forward voltage drop of both the diodes are 0.7 V. [15]



- A 220 V, 60 Hz voltage is applied to a centre tapped transformer with turns ratio of 22: 1 [5]  
with a load of 1 kΩ. If the resistance of half-secondary winding is 0.5 Ω, Determine:

  - peak, rms and dc voltages, 10V, 7.072V
  - peak, rms and dc currents, 10mA, 7.072mA

SEARCH VIT QUESTION PAPERS  
ON TELEGRAM TO JOIN



- (c) dc power delivered to the load  $5.7 \text{ mW}$   
 (d) ripple factor  $1.9\%$   
 (e) What is the PIV of each diode?  $0.2 \text{ kV}$   
 Assume diodes to be ideal.

4. The circuit shown in Fig. 4 is operating at point  $Q_2$  in the active region. Find the values of  $V_{CC}$  and  $V_{BB}$  to move the  $Q$  point from  $Q_2$  to  $Q_1$  ( $V_{CE} = 2.3 \text{ V}$  and  $I_C = 3.7 \text{ mA}$ ). [10]  
 $9.7 \quad 5.1$

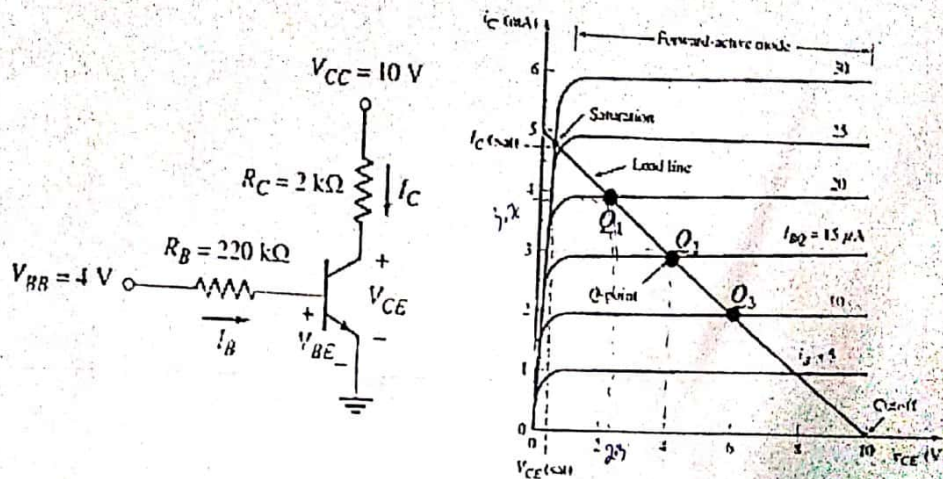


Fig. 4

5. Construct the voltage divider bias network in Fig. 5 to establish a current  $I_E = 5 \text{ mA}$  using a power supply  $V_{CC} = 12 \text{ V}$ ,  $\beta = 50$ . [10]

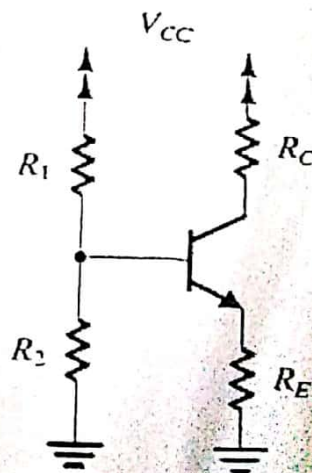


Fig. 5

SEARCH IIT QUESTION PAPERS  
 ON TELEGRAM TO JOIN