

Faculty of Science & Technology

First Semester B.Tech. (ET in ET) (Common) (NEP) (AI/AIDS/AIML/RoAI/I IOT)

2024-2025 Examination

DIGITAL CIRCUITS & LOGIC DESIGN

Time : Three Hours]

[Maximum Marks : 70

INSTRUCTIONS TO CANDIDATES

- (1) All questions carry marks as indicated.
- (2) Solve Question No. 1 ~~OR~~ Question No. 2.
- (3) Solve Question No. 3 ~~OR~~ Question No. 4.
- (4) Solve Question No. 5 ~~OR~~ Question No. 6.
- (5) Solve Question No. 7 ~~OR~~ Question No. 8.
- (6) Solve Question No. 9 ~~OR~~ Question No. 10.
- (7) Due credit will be given to neatness and adequate dimensions.
- (8) Assume suitable data whenever necessary.
- (9) Illustrate your answers whenever necessary with the help of neat sketches.

1. (a) Explain different types of gates used in digital systems. 7
- (b) Simplify using K-map and realize using gates :

$$f(A, B, C, D) = \sum m(0, 1, 4, 5, 9, 11, 14, 15) + \sum \phi(10, 13).$$
 7

OR

2. (a) Explain and prove De-Morgan's Theorem. 6
- (b) Solve the following :
 - (i) $(1101.11)_2 = ()_{10}$
 - (ii) $(12.625)_{10} = (?)_2$
 - (iii) $(356)_{10} = (?)_8$
 - (iv) $(5352.4051)_8 = (?)_{10}$ 8

3. (a) Implement a Full Adder using two Half Adder and OR gate. 7
 (b) Design a 4 bit BCD adder 7

OR

4. (a) Implement 1 : 16 De multiplex using two 1 : 8 de multiplexers. 7
 (b) Implement the following function using 8 : 1 multiplexer :
 $F = \sum m(0, 1, 2, 3, 11, 12, 14, 15).$ 7
5. (a) Draw and explain Master Slave JK flip flop. 6
 (b) Convert :
 (i) JK flip flop to T flip flop
 (ii) JK flip flop to D flip flop. 8

OR

6. (a) What do you mean by Race around condition in JK flip flop ? How this condition can be overcome ? 7
 (b) Draw and Explain D type flip flop. 7
7. (a) Differentiate between Synchronous & Asynchronous counters. What do you mean by a modulus of counter ? 7
 (b) Design a 4 bit up/down asynchronous counter circuit. 7

OR

8. (a) Explain Serial Input Parallel Output (SIPO) Shift Register. 7
 (b) Differentiate between Mealey and Moore Machines. 7
9. (a) Write a note on PAL. 7
 (b) Write a note on Dynamic memories. 7

OR

10. (a) Write a note on Optical Disk. 7
 (b) Write a note on Static Memories. 7