



# MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY, WEST BENGAL

Paper Code : PC-EE501/PC-EE504/PC-EEE504 Power Electronics

UPID : 005526

Time Allotted : 3 Hours

Full Marks :70

The Figures in the margin indicate full marks.

Candidate are required to give their answers in their own words as far as practicable

## Group-A (Very Short Answer Type Question)

1. Answer any ten of the following : [ 1 x 10 = 10 ]
- A single phase diode bridge rectifier supplies a highly inductive load. The load current can be assumed to be ripple free. What will be the ac supply side current waveform?
  - The fundamental component of output voltage for a half wave bridge inverter (with a DC voltage source of magnitude is  $V_s$ ), is given by.....
  - What is series resonant inverter?
  - HVDC power transmission system is economical for.....as compared to AC transmission
  - What are holding and latching currents in SCR?
  - For high frequency applications of over 10 kW power rating, ..... type of diodes are used
  - How to protect an SCR against  $di/dt$ ?
  - What is dual converter?
  - A 3 phase VSI (Voltage source inverter) is supplied from a 600V DC source, and is connected to a star connected load of  $20 \Omega$  per phase. The load power in (kW) for 120 degree mode of conduction is .....
  - What is ZVS resonant converter?
  - The range of firing angle used in a thyristor controlled reactor (TCR) is.....
  - The two six pulse converters are connected in series on the dc side to meet the .....requirements in HVDC systems

## Group-B (Short Answer Type Question)

Answer any three of the following : [ 5 x 3 = 15 ]

- Write a short note on HVDC links. [5]
- What are the different types of power diodes? [5]
- Explain the two transistor analogy of an SCR. [5]
- Explain the operation of a single phase half wave controlled rectifier. [5]
- Explain the effect of source inductance in a single phase fully controlled rectifier. [5]

## Group-C (Long Answer Type Question)

Answer any three of the following : [ 15 x 3 = 45 ]

- Explain the working principle of three phase fully controlled bridge rectifier with highly inductive load. [ 5 ]
  - A single-phase full-bridge inverter, fed from 230 V dc, is connected to load  $R=10 \Omega$  and  $L=0.03$  H. For the square wave output of 50Hz frequency, find the following: [ 8 ]
    - The RMS value of fundamental voltage
    - Load impedance ( $\Omega$ ) at fundamental frequency
    - The RMS value of fundamental component of load current
    - The maximum voltage to be blocked by each device when it is in OFF condition
  - What is displacement power factor? [ 2 ]
- Explain the working principle of single phase half bridge inverter. [ 5 ]
  - A single-phase half bridge inverter has a load resistance  $R=2\Omega$ , and a DC voltage source  $V_s = 230$  V. What is the RMS value of the fundamental component of output voltage and the load current? [ 7 ]
  - What is feedback diode? [ 3 ]
- Discuss how resonant converters are classified.. [ 12 ]
  - What are the applications of series resonant inverters? [ 3 ]

10. (a) Explain the speed control technique of a thyristor fed ac motor. [ 8 ]  
(b) Explain the types of power converter topologies used in HVDC transmission system. [ 7 ]
11. (a) What are the different turn on process of an SCR? [ 6 ]  
(b) Explain a suitable snubber circuit for an SCR with a neat sketch and necessary equations. [ 5 ]  
(c) Define reverse recovery time of an SCR with necessary equations. [ 4 ]

\*\*\* END OF PAPER \*\*\*