
 


 

Answer any TEN Questions
(10 X 10 = 100 Marks)


1. a) Simplify the following Boolean Expression using K-Map. [2.5]
 $F(a,b,c,d) = \prod(2,4,9,12,15) + d(3,5,6,13)$
 b) Draw the logic circuit for the derived expression and find the NOR equivalent for the same. [2.5]
 c) Represent the following expression in Sum of minterms and Product of maxterms. [5]
 $A' + B' + A'C + ABCD$
2. Refer to Figure below, where an analog-to-digital converter is monitoring the dc voltage (V_B) of a 12-V storage battery on an orbiting spaceship. The converter's output is a four-bit binary number, ABCD, corresponding to the battery voltage in steps of 1 V, with A as the MSB. The converter's binary outputs are fed to a logic circuit that is to produce a HIGH output as long as the binary value is greater than 01102=610; that is, the battery voltage is greater than 6 V. Design this logic circuit using 4*1 multiplexer. [10]
3. In digital systems it is often necessary to have circuits that can shift the bits of a vector by one or more bit positions to the left or right. Design a combinational circuit using decoder and external OR gates that can shift a four-bit vector $W=w_3w_2w_1w_0$ one bit position to the right when a control signal Shift is equal to 1. Let the outputs of the circuit be a four-bit vector $Y=y_3y_2y_1y_0$ and a signal k, such that if Shift=1 then $y_3=0, y_2=w_3, y_1=w_2, y_0=w_1$, and $k=w_0$. If Shift=0 then $Y=W$ and $k=0$. [10]
4. The below circuit shows a sequential circuit that uses two D-flip flops and two multiplexers. There are three inputs to the circuit, namely A_0, A_1 and S. The input C is the clock and the state variables Q_1 and Q_0 are the output of the circuit. At time t_0 , the output values $Q_1=0$ and $Q_0=1$. Show the timing diagram for the state variables Q_1 and Q_0 . Also derive the state diagram and state table. [10]



JOIN
VIT QUESTION PAPERS
ON TELEGRAM



 5. Draw the timing diagram for this circuit until 10 clock pulses, assuming all Q outputs begin in the low state. Also give the table for 7 shifts at each clock pulse. [10]



6. Design an Asynchronous counter which counts in the sequence 001, 011, 101, 110, 010, 111, 000, 001 ... [10]
using JK Flip Flop. Remodify the same for working as a down counter.
7. a) Analyse the following instructions and specify the content of flag registers, general purpose register and accumulator at the end of execution of every instruction. [5]
- ```

MVI A, #29H
MVI B, #30H
MOV C, B
ADC B
MOV D, A
SBB C
MOV E, A
HLT

```
- b) Calculate the execution time for each Machine cycle and the instruction if the clock frequency  $f=7$  MHz. [5]
- MVI B, #09H
  - CMA
  - ADI #07H
8. Analyse the use of the following instructions and specify the Addressing modes used. [10]
- MOV AX, DX
  - MOV BX, [1345H]
  - MOV CX, [BX]
  - MOV DX, [BX + SI + 0AH]
  - MOV SI, [1234H]
9. a) Write an assembly language program using 8086 instructions for finding the LCM for two numbers stored in memory location 2034H and 2035H. Store the result in the memory location 1034H. [5]
- b) Elucidate an assembly language program for finding the factorial of a number in 8086. [5]
10. Illustrate how the serial data communication could be carried out by the microprocessor using peripheral chip with a neat architectural diagram. [10]
11. a) Analyse the need of FPGA in digital design. [5]
- b) Discuss how Internet of Things could be helpful in Industrial Automation. [5]

