

DIGITAL SYSTEMS DESIGN
(ECEN 2002)

Time Allotted: 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

Group – A
(Multiple Choice Type Questions)

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) The binary number 10101 is equivalent to decimal number
(a) 19 (b) 12 (c) 27 (d) 21.
 - (ii) The inputs of a NAND Gate are connected together. The resulting circuit is
(a) OR Gate (b) AND Gate
(c) NOT Gate (d) None of the above.
 - (iii) The only function of NOT Gate is to
(a) Stop signal (b) Invert input signal
(c) Act as a Universal Gate (d) None of the above.
 - (iv) A device which converts BCD to seven segments is called
(a) Encoder (b) Decoder
(c) Multiplexer (d) None of these.
 - (v) In the expression $A + BC$, the total number of Minterms will be
(a) 2 (b) 3 (c) 4 (d) 5.
 - (vi) A Full Adder can be made out of
(a) Two Half Adders
(b) Two Half Adders and an OR Gate
(c) Two Half Adders and a NOT Gate
(d) Three Half Adders.

- (vii) The basic storage element in a digital system is
(a) Flip Flop (b) Counter
(c) Multiplexer (d) Encoder.
- (viii) Don't care conditions can be used for simplifying Boolean expressions in _____
(a) Registers (b) Terms
(c) K-maps (d) Latches
- (ix) The speed of conversion is maximum in
(a) Successive-Approximation A/D Converter
(b) Parallel-Comparative A/D Converter
(c) Counter Ramp A/D Converter
(d) Dual-Slope A/D Converter.
- (x) Which of the following is the fastest logic?
(a)TTL (b)ECL (c)CMOS (d)LSI

Group – B

2. (a) (i) State the distributive property of Boolean algebra.
(ii) Prove that $ABC + ABC' + AB'C + A'BC = AB + AC + BC$
- (b) (i) Design XNOR Gate using NAND Gates only.
(ii) Design a full subtractor circuit using logic gates.
- 5 + 7 = 12**
3. (a) Draw the logic diagram of full adder and explain its operation.
- (b) Using 8 to 1 multiplexer, realize the Boolean function
 $T = f(w, x, y, z) = \Sigma(0,1,2,4,5,7,8,9,12,13)$
- 6 + 6 = 12**

Group – C

4. (a) Implement a 2-Bit Comparator Circuit.
- (b) Explain the BCD number and Implement a BCD Adder Circuit.
- 5 + 7 = 12**
5. (a) Implement a 9-Bit Odd/Even Parity Generator-cum-Checker Circuit.
- (b) Briefly describe the design of SRAM and DRAM.
- 4 + 8 = 12**

Group – D

6. (a) (i) Distinguish between a combinational logic circuit and a sequential logic circuit.
(ii) Define Flip flop.
- (b) Realize a JK flip flop using SR flip flop.

4 + 8 = 12

7. (a) Design a 4-Bit Synchronous Up and Down Counter.
- (b) Design a Four-bit register using D Flip Flop.

6 + 6 = 12

Group – E

8. (a) Design a 4-Bit R-2R Ladder Type Digital-to-Analog Converter.
- (b) Design a 4-Bit Flash Type Analog-to-Digital Converter.

6 + 6 = 12

9. (a) Explain the point/points of Superiority of CMOS Logic over other Logic Families.
- (b) Design a PMOS NOR and a NAND gate.

4 + 8 = 12

Department & Section	Submission Link
IT	https://classroom.google.com/c/MTg0NTYwNzA0ODUy/a/Mjc0MDY4MTk1MzAy/details

Department & Section	Submission Link (Backlog)
IT	https://classroom.google.com/c/Mjg2Mjg3Njl1MDg2?cjc=ueqyxmy

