

[No. of Printed Pages – 4]

ES201

Enrol. No.

[ET]

END SEMESTER EXAMINATION : NOV.-DEC., 2018

BASIC ELECTRONICS ENGINEERING

Time : 3 Hrs.

Maximum Marks : 70

Note: Attempt questions from all sections as directed.


Use of Scientific calculator is allowed.

SECTION – A (30 Marks)

Attempt any five questions out of six.



Each question carries 06 marks.

 1. Explain base-width modulation (the Early effect) with the aid of plots of potential and minority concentration throughout the base region.
2. (a) Design a clamper that will perform following function : (3)



P.T.O.

  (b) Determine V_o for the following network : (3)



3. Consider an operational amplifier in which the first set of signals is $v_1 = +50 \mu\text{V}$ and $v_2 = -50 \mu\text{V}$ and the second set is $v_1 = 1050 \mu\text{V}$ and $v_2 = 950 \mu\text{V}$. If the common-mode rejection ratio is 100, calculate the percentage difference in output voltage obtained for the two sets of input signals.
4. Give the significance of virtual ground in an op-amp. Also derive the following expression :

$$V_o = A_d V_d \left(1 + \frac{1}{\text{CMRR}} \frac{V_c}{V_d} \right)$$

5. (a) Explain the significance of diffusion capacitance and derive expression for the same. (3)
- (b) Reduce the following function to its minimum SOP form :

$$Z = A'B'C'D' + A'B'CD' + AB'C'D' + A'BCD + AB'CD' + A'B'CD$$
 (3)


6. (a) The RC coupling amplifier gives constant gain over the mid frequency range. Explain. (3)
- (b) Derive an expression for Transformer Utilization Factor (TUF) for the half wave rectifier. (3)

SECTION - B (20 Marks)

Attempt any two questions out of three.

Each question carries 10 marks.

 7. (i) Design the network of the given figure to maintain V_L at 12 V for a load variation (I_L) from 0 to 200 mA. Calculate the R_s and V_Z .



- (ii) Determine P_{zmax} for the Zener diode of part (i).

8. (a) Explain the meaning of pinch-off voltage in a JFET. Sketch the circuit of source follower and explain its working. Also determine its output impedance. (5)
- (b) The common drain circuit has $R_1 = 3.5 \text{ M}\Omega$, $R_2 = 1.5 \text{ M}\Omega$, $R_s = 2 \text{ k}\Omega$, $R_L = 20 \text{ k}\Omega$, $g_m = 2.5 \text{ mS}$. Determine input impedance, output impedance and voltage gain. (5)

P.T.O.


9. (a) Simplify the following using K-map and implement the simplified function using NOR gates :

$$Y = \prod M(0,1,5,9,13,14,15) + d(3,4,7,10,11). \quad (5)$$

- (b) Show that a full subtractor can be constructed using two half subtractors and an OR gate. Deduce a full adder using EX-OR gate. (5)

SECTION - C **(20 Marks)**
(Compulsory)

 10. (a) For the given voltage feedback network, determine I_C , V_C , V_{CE} , V_E : (10)



- (b) Discuss the operation of non-inverting amplifier and also derive the expression for its voltage gain. (5)
- (c) Derive the mathematical expression of transconductance for JFET. Also find $V_{GS(off)}$ if the $g_{mo} = 10 \text{ mS}$ and $I_{DSS} = 10 \mu\text{A}$. (5)