



Answer any TEN Questions  
(10 X 10 = 100 Marks)

1. Using nodal analysis, find  $V_1$  and  $V_2$  in the circuit shown in Fig.1

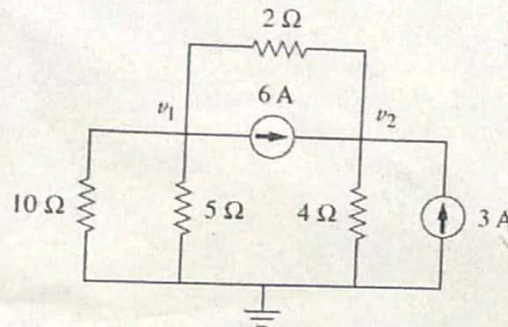


Fig.1

2. Find the  $P_{\max}$  delivered to load  $R_L$  for the circuit shown in Fig.2

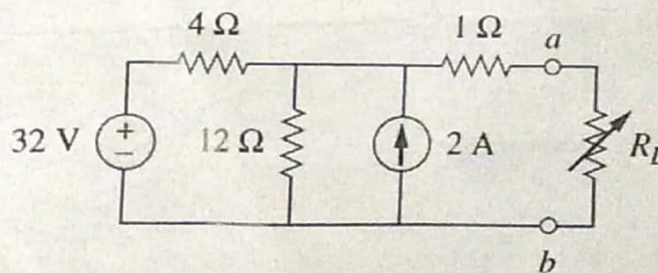


Fig.2

3. a) The instantaneous value of voltage in an AC circuit is given by  $V(t) = 100 \sin (50\pi t - 0.523) V$ . [5]  
Find (i) peak to peak voltage (ii) average voltage (iii) RMS voltage (iv) frequency and (v) phase angle
- b) A series RLC circuit with  $R=40 \Omega$  and  $L=50.07 \text{ mH}$  is connected across a 400 V, 50 Hz supply. The circuit draws a current of 10A. Find (i) capacitor value (ii) power factor of the circuit (iii)  $V_L$  and  $V_C$ . [5]
4. a) The power taken by an inductive circuit when connected to a 120 V, 50 Hz supply is 400 W and the current is 8A. Calculate (i) resistance (ii) impedance (iii) reactance (iv) power factor and (v) phase angle between voltage and current. [5]
- b) Deduce the condition for a RLC circuit to behave like a resistive circuit and mention the nature of following parameters at this condition. (i) Current (ii) Phase angle and (iii) power factor. [5]



5. Explain the construction and different types of DC generators in detail.
6. Explain the construction and principle of operation of Transformer in detail.
7. Design a circuit to add three bit numbers with two circuits adding two bit numbers.
8. Design a logic circuit which receives four bit binary number and gives out an output whenever the number is divisible by 4 or 5.
9. Explain the operation of BJT in common emitter configuration.
10. Design a Voltage regulator circuit to get 5 V DC output when the input is 20 V AC.
11. Find  $i_o$  using mesh current analysis for the circuit shown in Fig.3

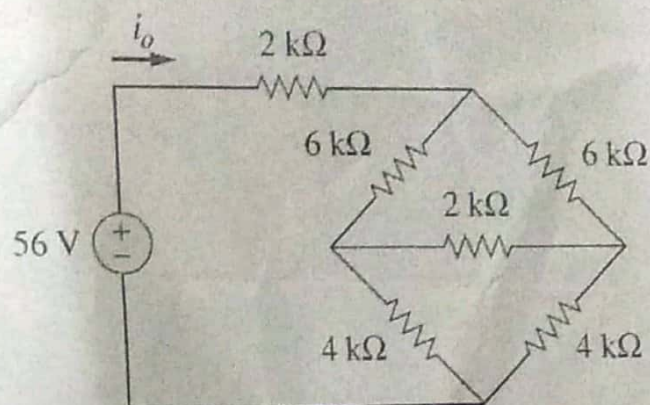


Fig.3

12. A coil of resistance  $5\ \Omega$  and inductance  $120\text{ mH}$  in series with a  $100\ \mu\text{F}$  capacitor is connected to a  $300\text{ V}$ ,  $50\text{ Hz}$  supply. Calculate (i) current flowing (ii) phase angle between the supply voltage and current (iii) voltage across the coil and (iv) voltage across the capacitor.



JOIN  
VIT QUESTION PAPERS  
ON TELEGRAM