

123105138

[ECPC-201]

**NATIONAL INSTITUTE OF TECHNOLOGY KURUKSHETRA**  
**THEORY EXAMINATION**  
**Question Paper**

**Month and Year: Nov/Dec 2024**

Semester 3<sup>rd</sup>

**Course No.: ECPC-201**

**Number of questions to be attempted: 05**

**Total no. of questions: 05**

**Programme: B.Tech. (ECE)**

**Subject: Electronic Devices and Circuits**

**Maximum marks: 50**

**Time allowed: 3 Hrs.**

No. of pages used: 02

**NOTE: Attempt all questions. Assume suitable data if required.**

Q.1(a) Discuss and differentiate between Avalanche and Zener breakdown mechanism. Also draw diode equivalent circuit models. [5]

(b) Determine the currents  $I_1$ ,  $I_2$ , and  $I_{D2}$  for the network of Fig. 1. [5]

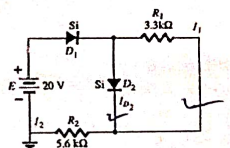


Fig. 1


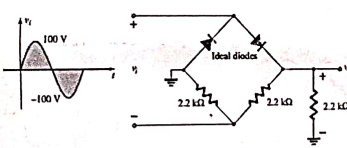
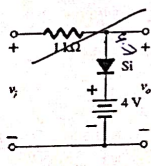



Fig. 2

Q. 27(a) Sketch  $V_0$  for the network of Fig. 2 and determine the dc voltage available. [5]

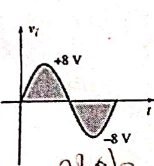(b) Determine  $V_0$  for each network of Fig. 3 for the input shown. [5]



(a)  
Fig. 3

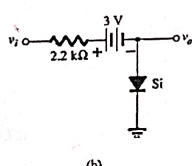

(b)

$$0.7 - I_1 R_1 = 0$$

$$20 - 0.7 - 0.7 - 1 (56W) = 0$$

[ECPC-201]

Q.3 (a) For the collector-feedback configuration of Fig. 4, determine:  $I_B$ ,  $I_C$  and  $V_C$ . [5]

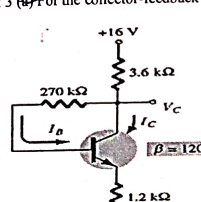


Fig. 4

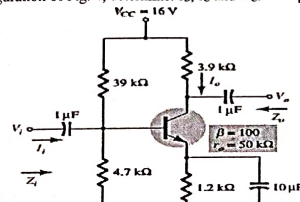


Fig. 5

(b) For the network of Fig. 5: [5]

(i) Determine  $r_e$  (ii) Find  $Z_i$  and  $Z_o$  (with  $r_o = \infty \Omega$ )  
(iii) Determine  $A_v$  (with  $r_o = \infty \Omega$ ) (iv) Repeat parts (iii) including  $r_o = 25 \text{ k}\Omega$ .

Q. 4 (a) Derive the expression of input impedance, output impedance, voltage gain and current gain of Common-Emitter configuration using complete hybrid model. [5]

(b) Explain the working of n-channel MOSFET stating depletion, weak and strong inversion conditions. Also draw the I-V characteristics. [5]

Q.5 (a) Derive the expression of input impedance output impedance, voltage gain of common-source MOSFET configuration. [5]

**OR**

(b) Explain the working of phase shift oscillator and derive the expression of frequency.

(c) Briefly explain the working of n-channel JFET. Also describe the following terms in connection to the MOSFET: [5]

- i. Channel length modulation
- ii. Drain Induced Barrier Lowering

\*\*\*\*\*