



SCHOOL OF ELECTRICAL ENGINEERING

CAT - I

Winter Semester 2018 - 19

Class Nbrs. : VL2018195001598,1862,3666,3667,3668,3669,3670,3672
Course Code : EEE1001
Course Title : Basic Electrical and Electronics Engineering
Programme Name & Branch: B.Tech , All branches

Date of Exam : 27/01/19
Max. Marks : 50
Duration : 1 ½ hours

General instruction: Answer all questions

S.No.	Question
1.	<p>Find the current through 100Ω resistor for the circuit shown in Fig.1 using mesh current method. [10]</p> <div data-bbox="510 896 1181 1254"></div> <p style="text-align: center;">Fig.1</p>
2.	<p>Determine the value of load resistor for the circuit shown in Fig.2, if maximum power is transferred. Also calculate the maximum power across the load resistor. [10]</p> <div data-bbox="303 1478 1372 1904"></div> <p style="text-align: center;">Fig.2</p>



3. Find the voltage across 30Ω resistor in the circuit shown in Fig.3 using nodal analysis. [10]

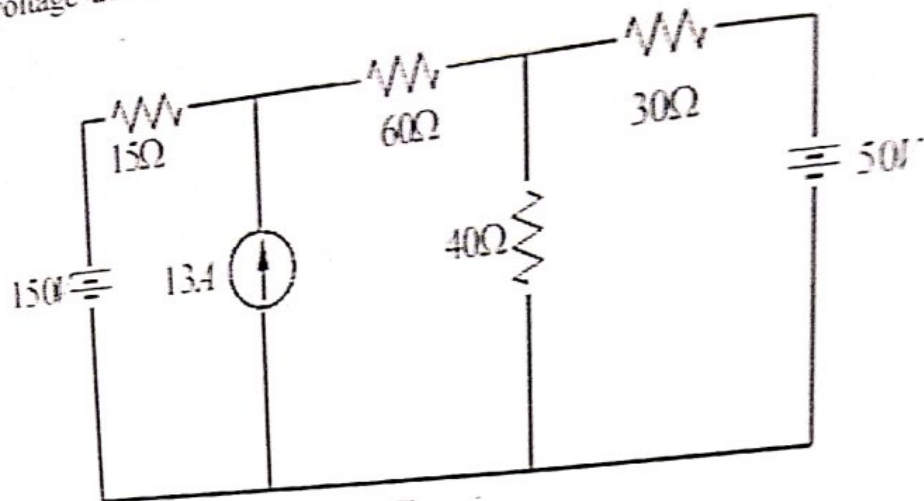


Fig. 3

4. i) Find the equivalent resistance in the circuit shown in Fig.4. [10]
ii) How much power is delivered by the source?

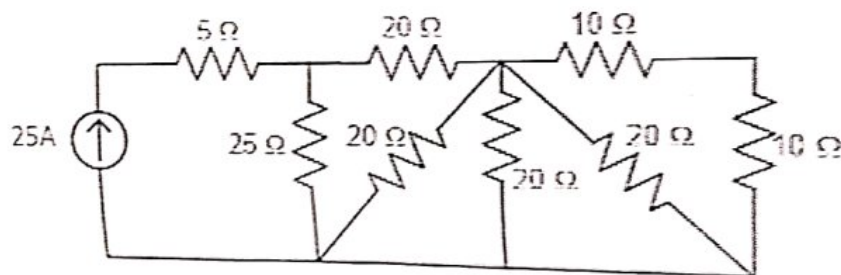


Fig.4

5. A 20Ω resistance and a 30mH inductance are connected in series and the circuit is fed from 230V , 50Hz , AC supply. Find inductive reactance, RMS value of current, voltage across resistance, voltage across inductance and power factor of the circuit. Draw the phasor diagram. [10]