



KEEPING MOBILE PHONE/SMART WATCH, EVEN IN 'OFF' POSITION, IS EXAM MALPRACTICE

Answer ALL Questions
(10 X 10 = 100 Marks)

1. Determine the mode of operation (saturation, linear, or cutoff) and drain current I_D for each of the biasing configurations given below. Verify with SPICE. Use the following transistor data: NMOS: $k'_n = 115 \mu A/V^2$, $V_{T0} = 0.43 V$, $\lambda = 0.06 V^{-1}$, PMOS: $k'_p = 30 \mu A/V^2$, $V_{T0} = -0.4 V$, $\lambda = -0.1 V^{-1}$. Assume $(W/L) = 1$ and neglect body effect.
 - a) NMOS: $V_{GS} = 2.5 V$, $V_{DS} = 2.5 V$. PMOS: $V_{GS} = -0.5 V$, $V_{DS} = -1.25 V$.
 - b) NMOS: $V_{GS} = 3.3 V$, $V_{DS} = 2.2 V$. PMOS: $V_{GS} = -2.5 V$, $V_{DS} = -1.8 V$.
2. a) Explain the following short channel effects
 - (i) Channel length modulation.
 - (ii) Body effect.
- b) Types of power consumption, dependence on V , f , and C . Write the equation for dynamic power consumption and the equation for static power consumption. Explain the circuit characteristics (e.g., V_t , temperature, or gate size) that each depends on.
3. a) What is the output function of the circuit shown in Fig.1

 


Fig.1



- b) Implement 1-bit comparator using PMOS PTL.
4. Implement $f(a, b, c, d) = ab'cd' + a'c' + dab$ using TG and NMOS pass transistors.
5. a) Sketch a 2-input NOR gate with transistor width chosen to achieve effective rise and fall resistance equal to a unit inverter. Compute the worst case rising and falling propagation delay of the NOR gate driving "h" identical NOR gates using the Elmore delay model. If $C = 2fF/\mu m$ and $R = 2.5K\Omega/\mu m$ in a 90nm process. What is the delay of a fanout of 3 NOR gates (2-input)?

[OR]

- b) Implement the following function as a single CMOS logic gate. Indicate the widths of all gates in terms of k , the minimal gate width. Size the transistors to achieve the same worst case resistance as a balanced minimal width inverter (i.e., an inverter with a k -wide NMOSFET and a $3k$ -wide PMOSFET). Estimate the rise and fall propagation delay of CMOS logic gate.

$$f(a, b, c, d) = \bar{a}(b\bar{c} + d)$$

$$f = 15RC$$

$$r = 33RC$$

6. Size the circuit given in Fig.2 for minimum delay. Show delay on each path.

 


Fig.2

7. a) Sketch a layout diagram for a CMOS gate computing the following expression and estimate the optimized area using lambda based rules.

$$Z = \overline{A+B+(C \cdot D)}$$

[OR]

7. b) Sketch the schematic for the layout shown in Fig.3. Determine the Boolean expression for the gate. Also estimate the optimized area using lambda rules.

 


Fig.3

$$\frac{2560\lambda^2}{(A+B) \cdot CD}$$

8. Consider the dynamic gate shown in the Fig.4. Based on the input signals draw the output signal. Implement the output function using DCVSL.

 


Fig.4

9. Design a negative edge triggered Master-Slave D-FF based on switching keys with asynchronous SET and RESET inputs. Explain its operation with timing diagram.

10. Design the 8 bit right barrel shifter using 2x1 Multiplexers.

